

CS 31007

Autumn 2021

COMPUTER ORGANIZATION AND ARCHITECTURE

Instructors

Rajat Subhra Chakraborty (*RSC*)

Bhargab B. Bhattacharya (*BBB*)

Lecture #26: Processor Design

27 September 2021

Indian Institute of Technology Kharagpur
Computer Science and Engineering

So far covered ...

- ❖ Introduction, CPU Performance Equation
 - ❖ MIPS Assembly Language
 - ❖ Number Systems: Integers, Floating-Point
 - ❖ Computer Arithmetic: Algorithms and Hardware
-
- ❖ Today: Moving into Processor Design ..

Building a Computer System



Courtesy: Satyajit Ray


Building a Computer System

CPU:

- Steering wheel of a computer system – Hardware realization
- Should be able to execute each instruction
- Arithmetic, data transfer, branch, etc. ..
- Coordinate among all modules
- Overall control of computing processes

Challenges

 - What are the issues in processor design?
cost, speed, capability, yield, portability, testing and fault-tolerance, security, IP-protection, market demand
- What are the inputs?
- What are the goals?
- What are the constraints?
 - cost, power, heat dissipation, silicon area, time-to-market
- How one can automate the entire design process?



Inputs

- ISA: Instruction Set Architecture
 - -- instruction sets, formats, addressing modes, register description, word length;
- Components: Basic ALU blocks: adders, multipliers ..
- Other logic blocks – MUX-es, Flip-Flops (FF)
- Register files, Program Counter (PC)
- Memory
- Clock for synchronizing FFs

Output

- Hardware design that is capable of executing instructions under program control

Issues

- CPU performance: IC, CPI, CCT
 - Instruction count (IC)
 - Determined by ISA and compiler
 - CPI and Clock Cycle time (CCT)
 - Determined by CPU hardware
- We will examine two MIPS implementations
 - A simplified version (single-cycle execution)
 - A more realistic and faster pipelined version
- Simple subset of ISA, covering most aspects
 - Memory reference: *lw, sw*
 - Arithmetic/logical: *add, sub, and, or, slt*
 - Control transfer: *beq, j*

Performance


- Execution Time = $IC * CPI * CCT$
- Processor design (datapath and control) will determine:

- Clock cycle time (CCT)

- Clock cycles per instruction (CPI)

Single-cycle processor:

 - Advantage: $CPI = 1$
- Disadvantage: long cycle time






Start with Designing a Simple ALU

- 1-bit ALU
- 32-bit ALU


An ALU (arithmetic logic unit)

   - Let's build an ALU to support `and`, `or`, `add`, `sub` (for integers) instructions
 - just build a 1-bit ALU, and use 32 of them



Implementation

 
- Let's look at a 1-bit ALU for addition:




$$C_{out} = ab + ac_{in} + bc_{in}$$
$$sum = a \oplus b \oplus c_{in}$$

- How could we build a 1-bit ALU for *add*, *and*, and *or*?

Building a 32-bit ALU (recall RCA)

 


1-bit ALU for performing
AND, OR, ADD

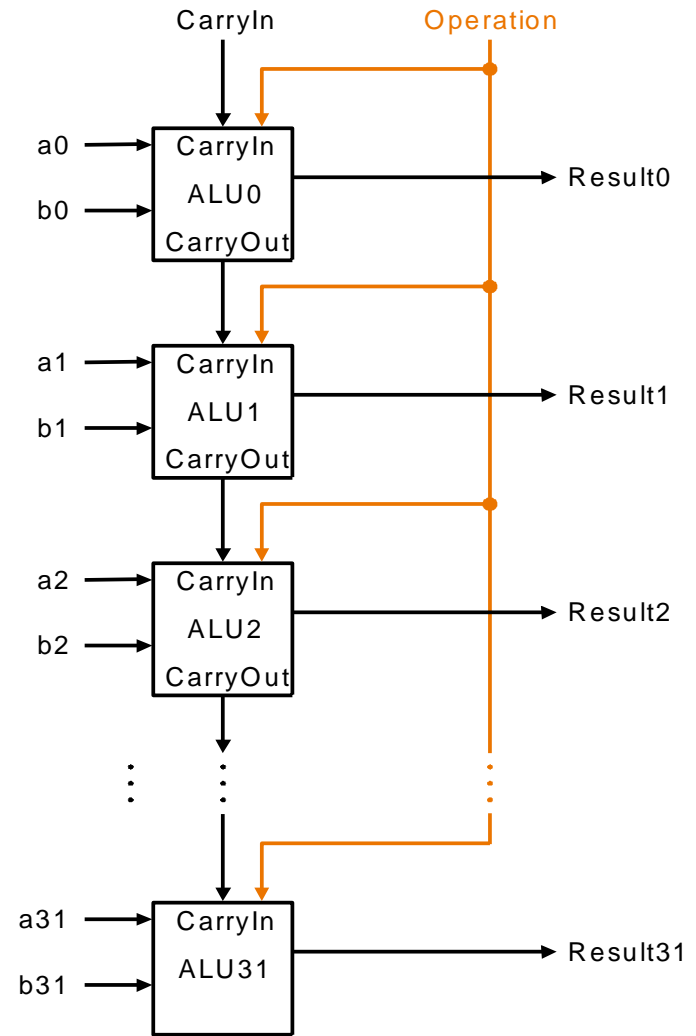

32-bit ALU for performing
AND, OR, ADD

Subtraction (a – b)

 - Two's complement approach: just negate b and add
=> set $Binvert = 1$; $Carry-in = 1$



1-bit ALU for performing
AND, OR, ADD, SUB

Adding other MIPS instructions to ALU

- Support the *set-on-less-than* instruction (*slt*)

■ `slt rd, rs, rt`

=> if ($rs < rt$), set $rd = 1$; else $rd = 0$;

=> use subtraction: $(rs - rt) < 0$ implies $rs < rt$

Support test for equality (`beq $t1, $t2, Label`)




=> use subtraction: $(\$t1 - \$t2) = 0$ implies $\$t1 = \$t2$

Supporting *slt* *rd*, *rs*, *rt*

slt:

if ($rs < rt$), set $rd = 1$; else $rd = 0$

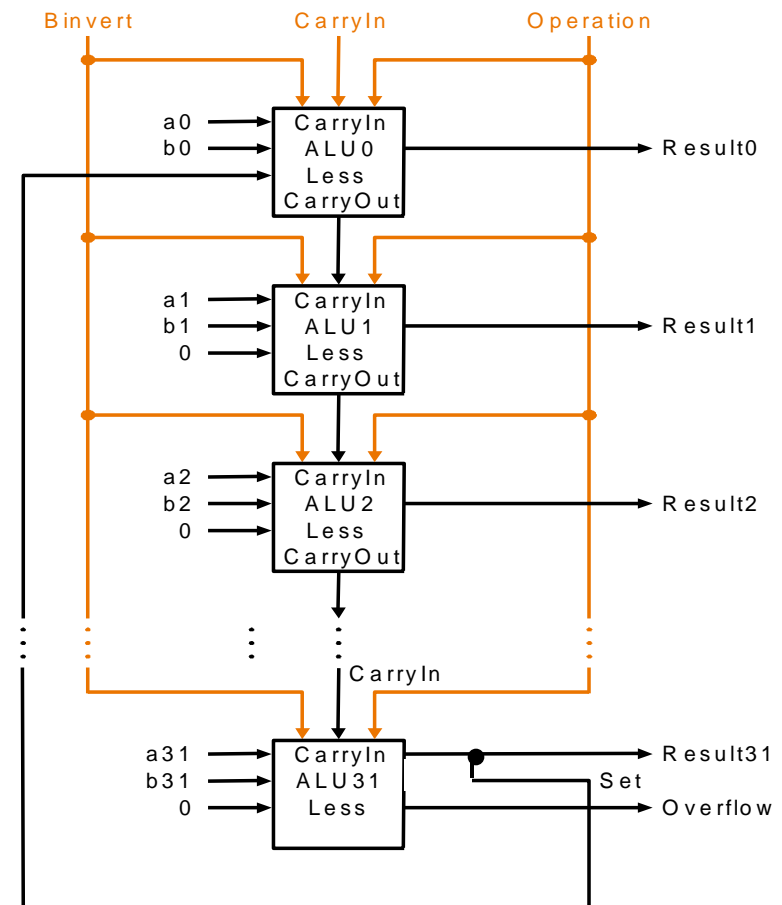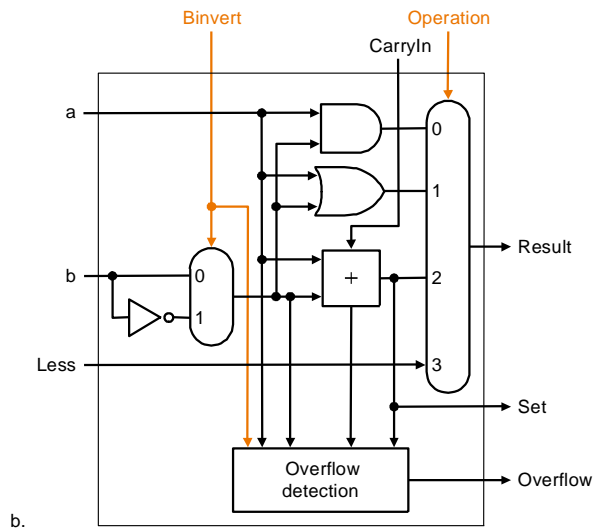 When the condition is true, i.e.
 $rs - rt < 0$ (negative) \Rightarrow
 rd : 00000001



Implementing *beq* \$t1, \$t2, Label

- Notice control lines:

000 = and

001 = or

010 = add


110 = subtract

111 = slt

output **Zero** becomes 1


when *beq* is taken;

PC needs to be updated ...

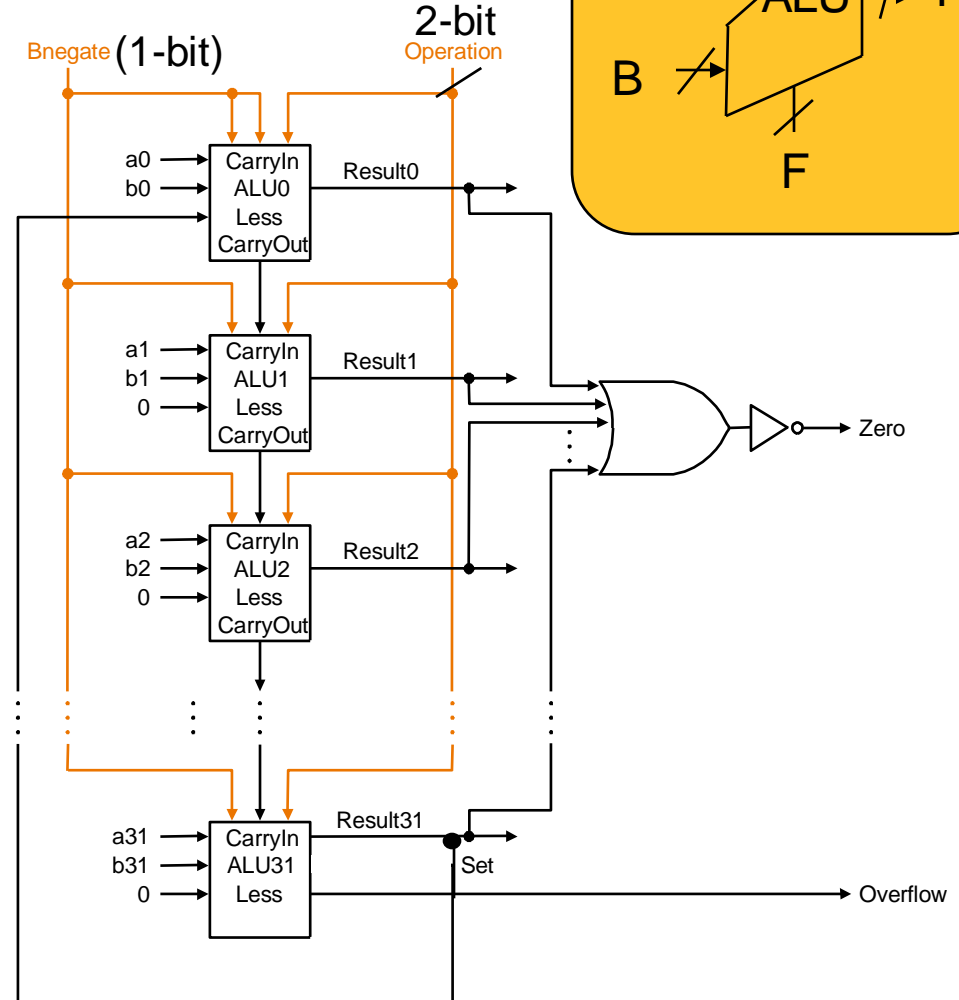

This ALU implements MIPS *add*, *sub*, *and*, *or*, *slt*, and *beq*

Recap: Execution Cycle (MIPS)

 

Obtain instruction from memory **(IF)**

Instruction-Decode and Register-Read **(ID/RR)**

CPU Design: Needs hardware implementation of all steps

Execute the instruction **(Ex)**

Locate and obtain operand data from memory/register **(Mem)**

Write-Back results in register/memory for later use **(WB)**


Determine successor instruction

IF → ID/RR → EX → Mem → WB

Instruction Execution


- PC → instruction memory, fetch instruction
- Register numbers → register file, read registers
- Depending on instruction class
 - Use ALU to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
 - Access data memory for load/store
 - $PC \leftarrow \text{target address or } PC + 4$

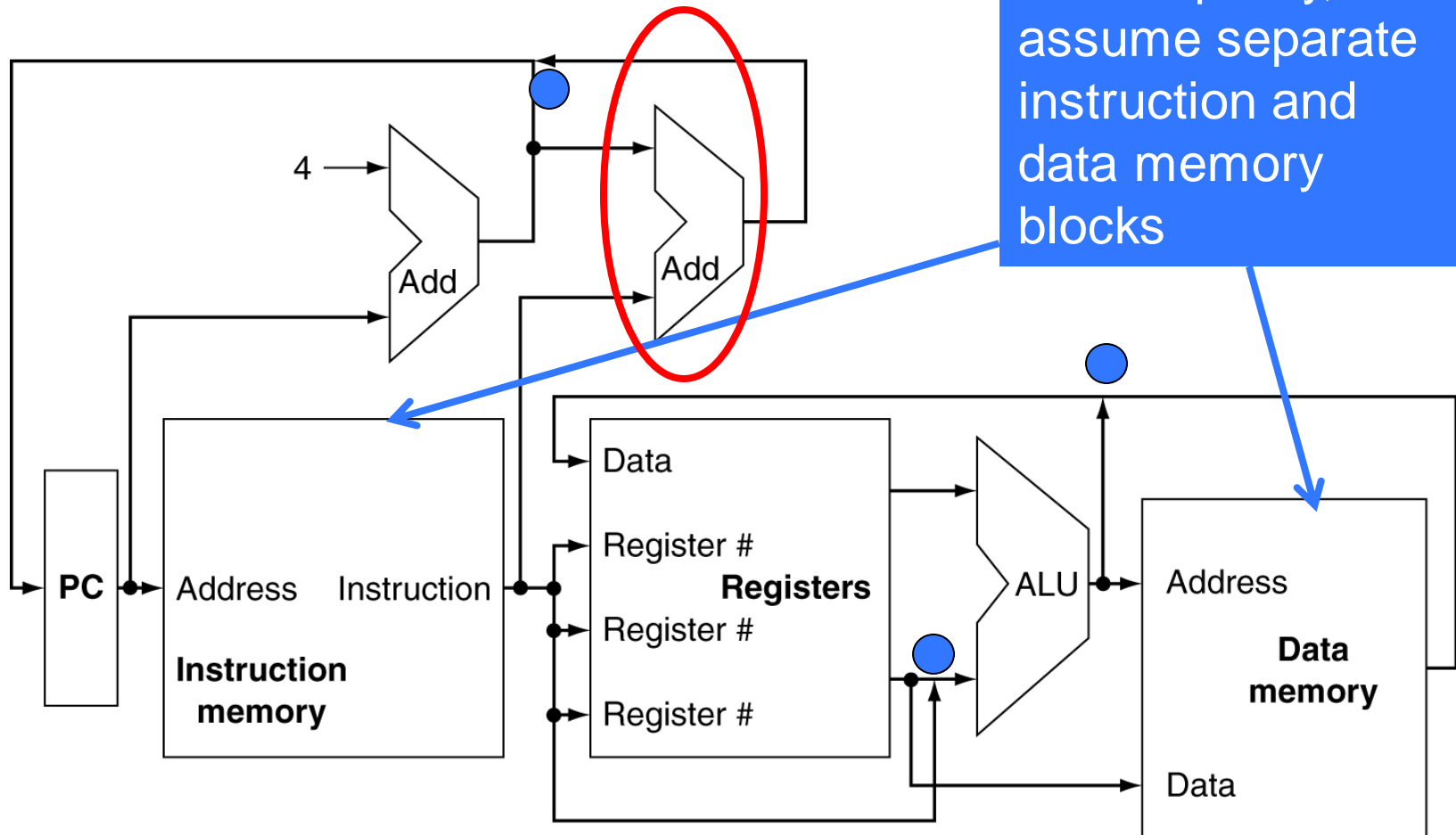CPU Overview: Fixing data and control paths




Two types of functional units:

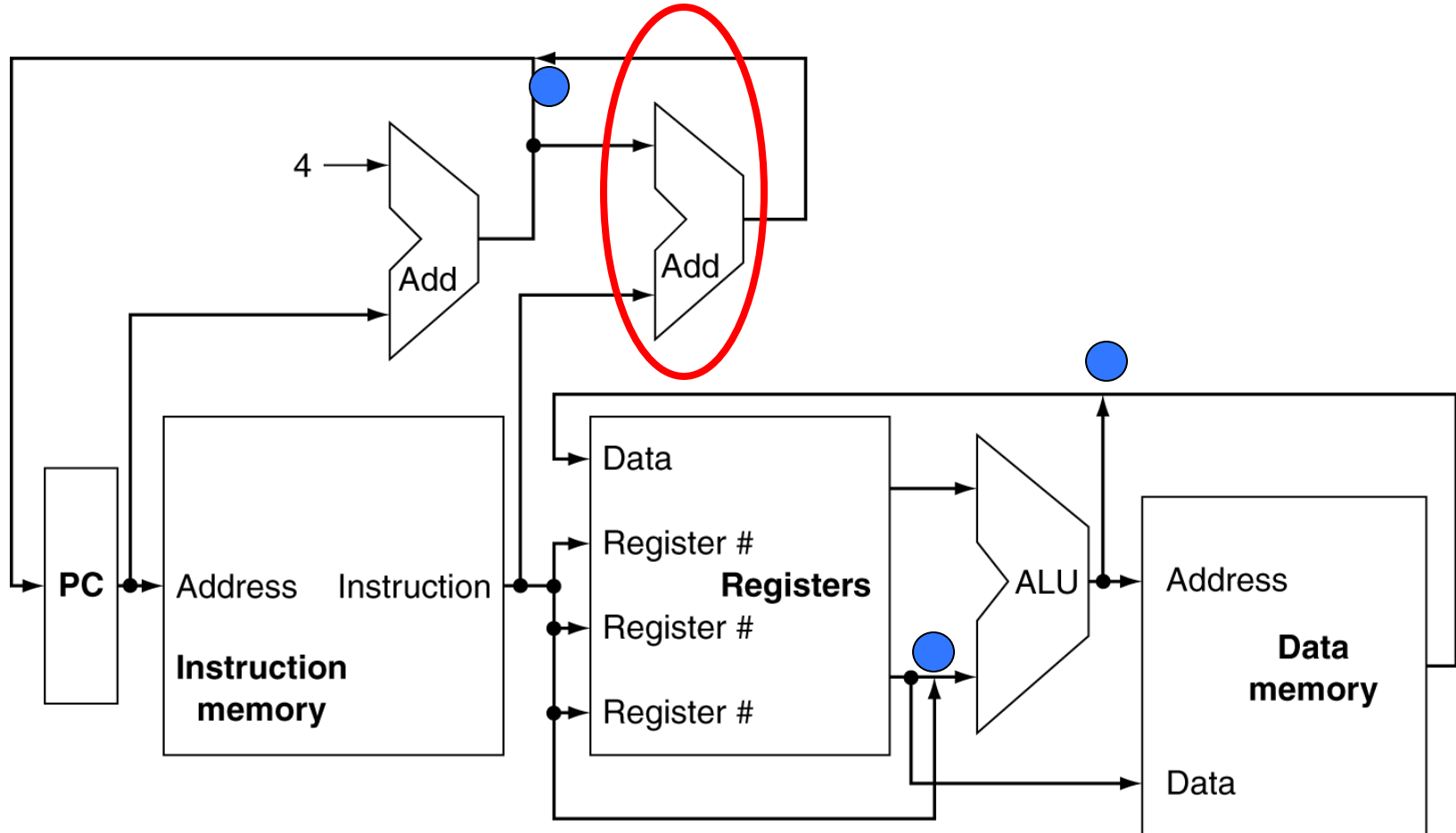- elements that operate on data values (combinational)
- elements that contain state (sequential)



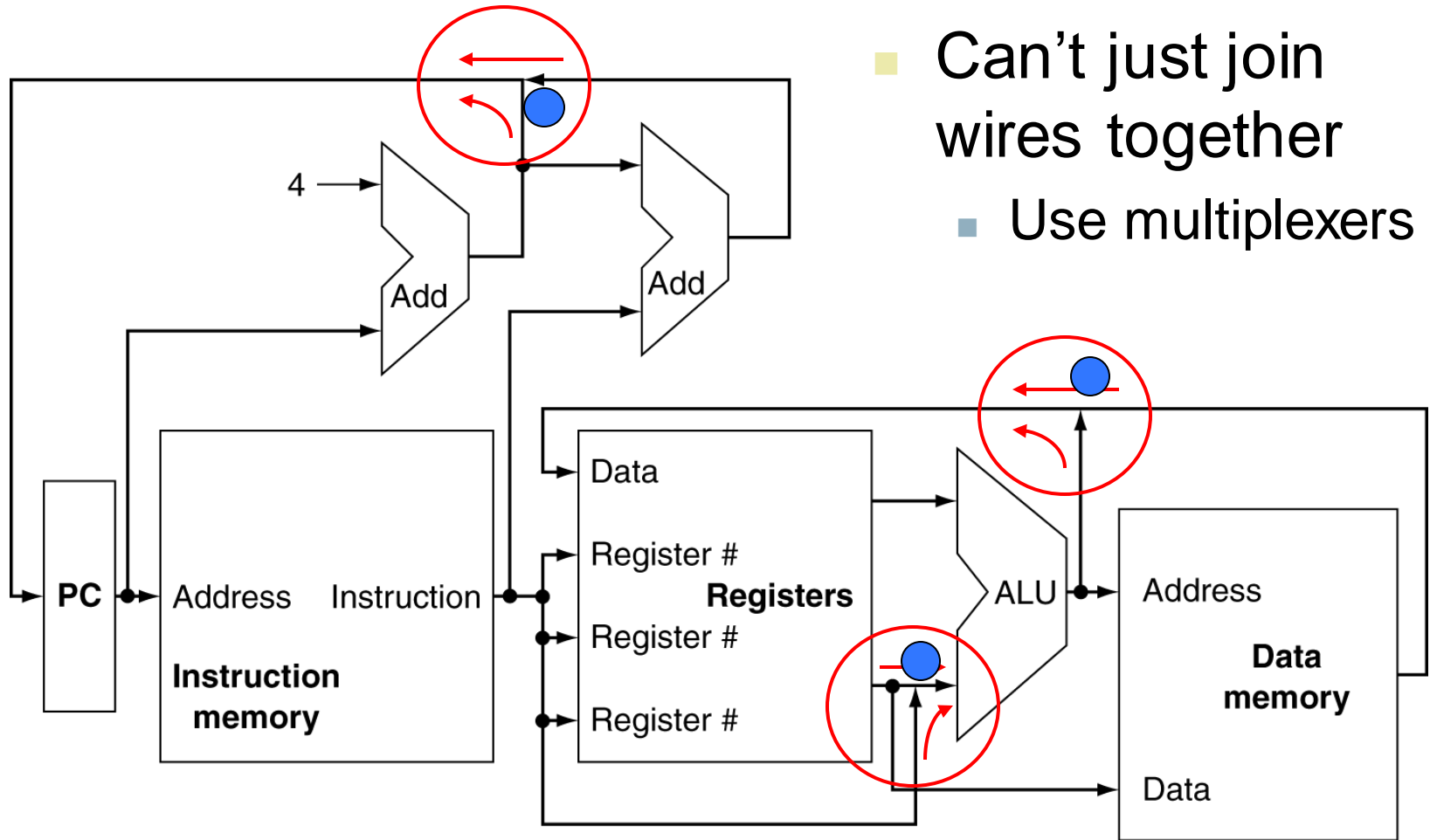
Multiplexers for stitching multiple paths



- Can't just join wires together
 - Use multiplexers

Control


IF → ID/RR → EX → Mem → WB

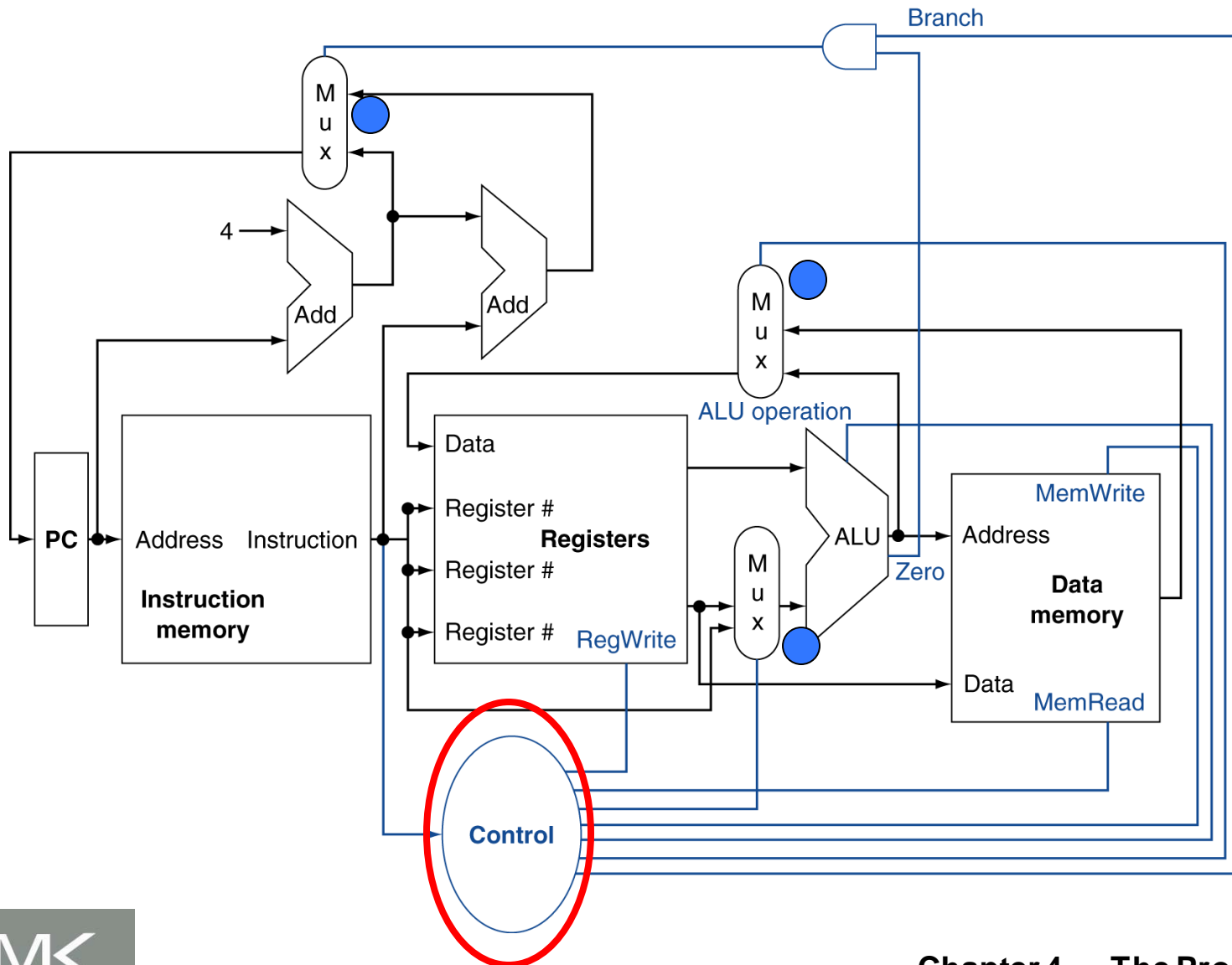


Combinational Elements

- AND-gate

- $Y = A \& B$

 


- Multiplexer

 


- Adder

- $Y = A + B$

 



- Arithmetic/Logic Unit

- $Y = F(A, B)$

 



Sequential Elements

  - Register: stores data in a circuit
 - Uses a clock signal to determine when to update the stored value
 - Edge-triggered: update when Clk changes from 0 to 1




Sequential Elements

  - Register with **write control**
 - Only updates on clock edge when write control input is 1
 - Used when stored value is required later



Register File: Read

- Built using D flip-flops

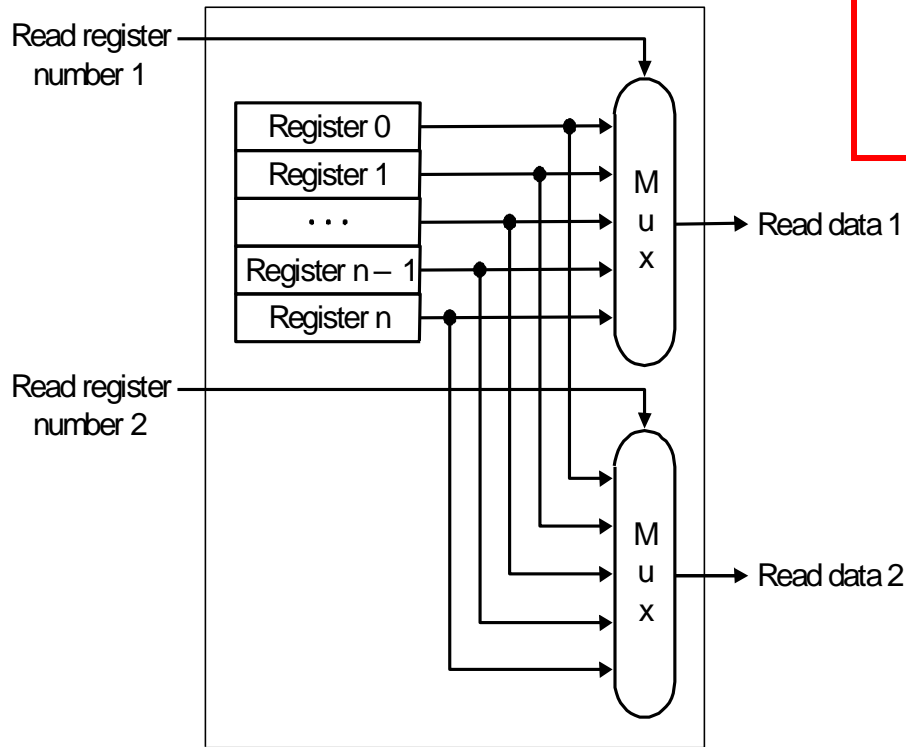


add rd, rs, rt

MIPS has a 32×32 -bit register file
Use for frequently accessed data
Numbered 0 to 31

Assembler names


\$t0, \$t1, ..., \$t9 for temporary values

 \$s0, \$s1, ..., \$s7 for saved variables



Register File: Write

 - use the clock to determine when to write, provided *Write* is enabled



add rd, rs, rt

CS 31007

Autumn 2021

COMPUTER ORGANIZATION AND ARCHITECTURE

Instructors

Rajat Subhra Chakraborty (*RSC*)

Bhargab B. Bhattacharya (*BBB*)

Lecture #27, #28

Single-Cycle Processor Design






28 September 2021

Indian Institute of Technology Kharagpur
Computer Science and Engineering

Simple Hardware Implementation of a CPU

- Functional units we need for implementing instructions

32-bit

   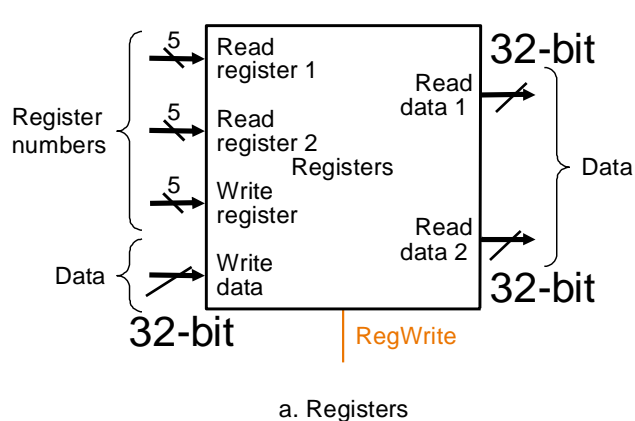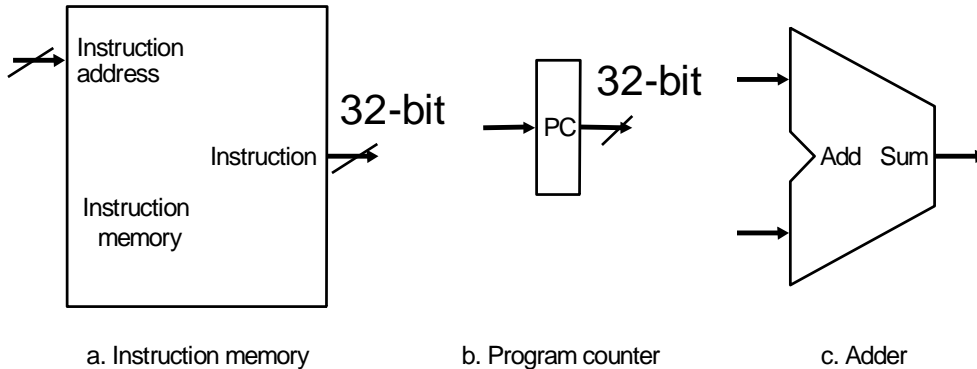

Building a Datapath

- Datapath
 - Elements that process data and addresses in the CPU
 - Registers, ALUs, mux's, memories, ...
- We will build a MIPS datapath incrementally
 - Refining the overview design

Processor Design



- We're ready to implement the MIPS “core”
 - load-store instructions: `lw`, `sw`
 - reg-reg instructions: `add`, `sub`, `and`, `or`, `slt`
 - control flow instructions: `beq`

First, we need to fetch an instruction into processor


- program counter (PC) supplies instruction address
- retrieve the instruction from memory

Accessing Instruction & Data in the Same Cycle?

 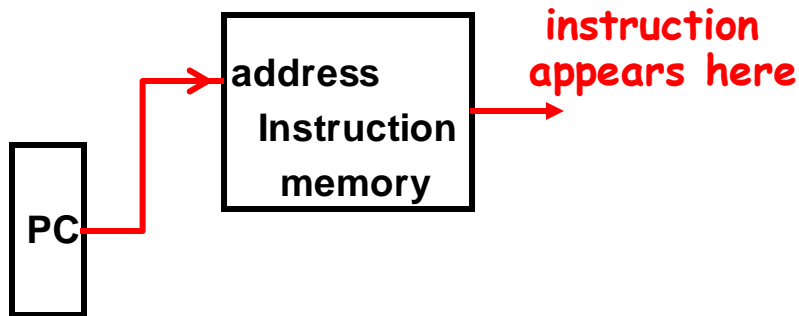Solution: Use separate instruction and data memory




Instruction Fetch

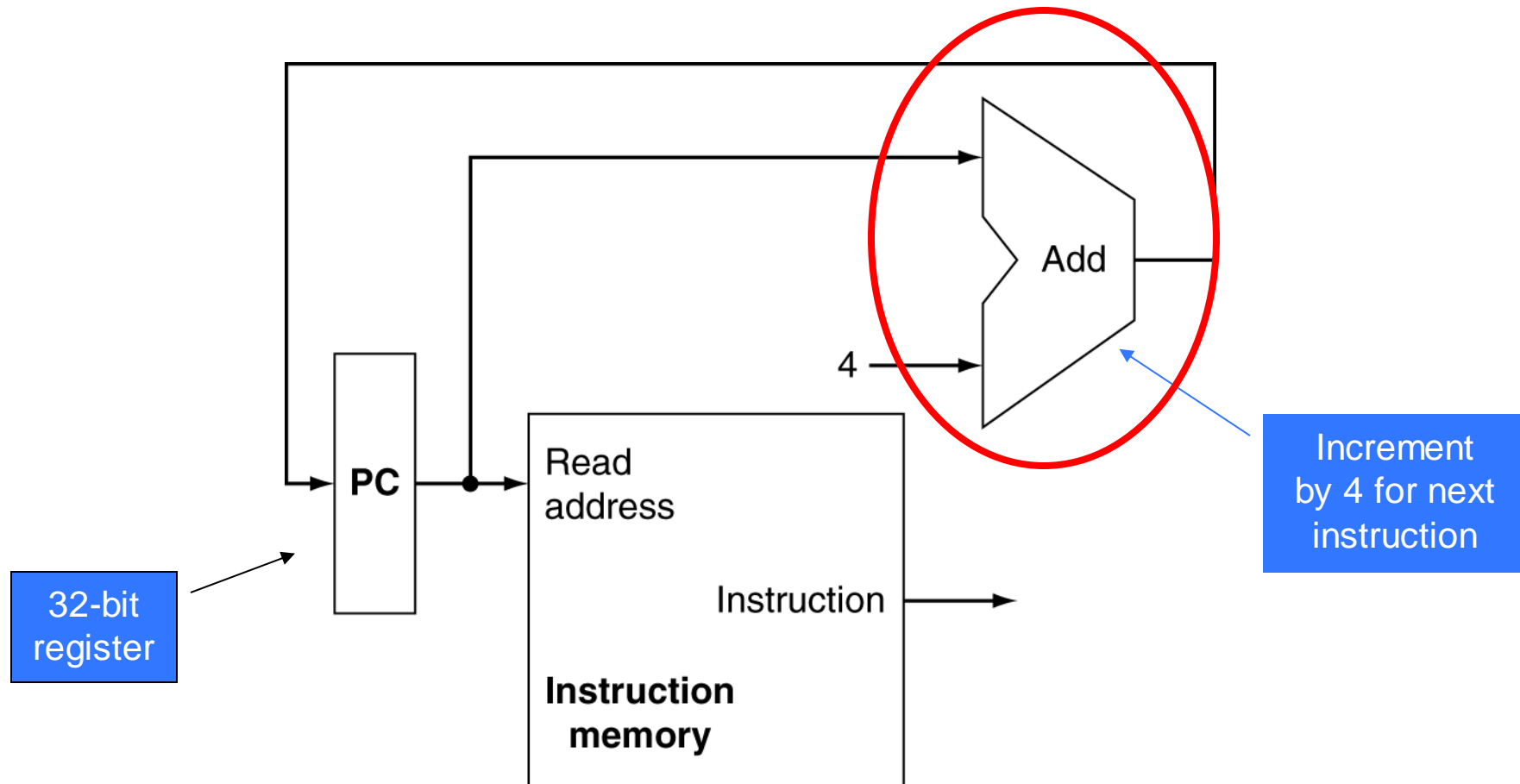

Instruction Fetch Unit

Updating the PC for next instruction

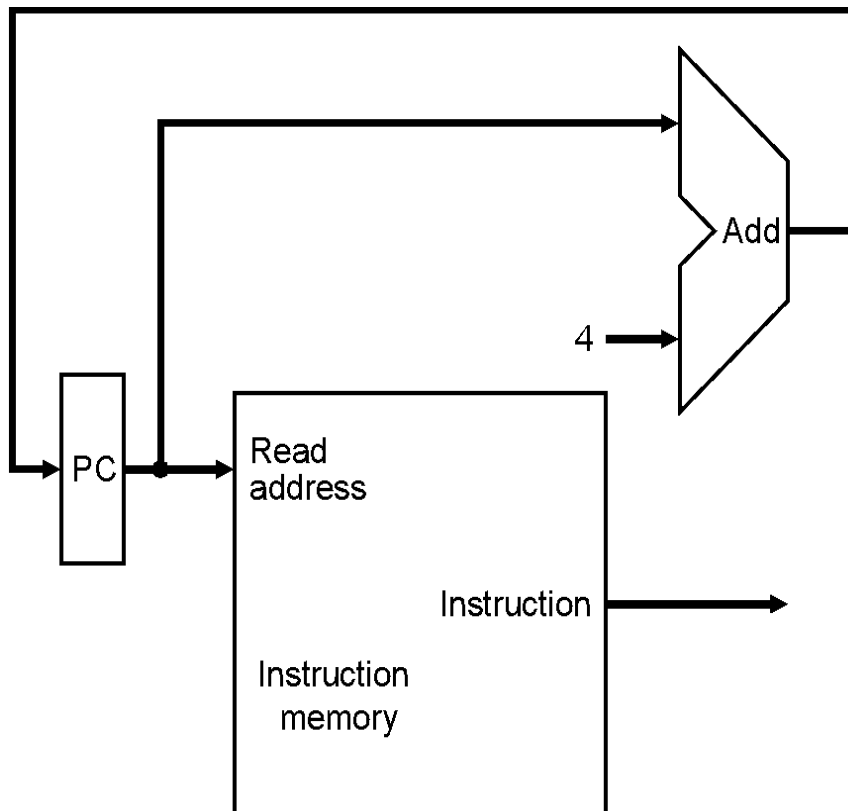
- Sequential Code: $PC \leftarrow PC + 4$
- **Branch and Jump: $PC \leftarrow$ “target address”**
(to be fixed later)



MIPS Instruction Subset

- **R-type**


- *add rd, rs, rt*
- *sub, and, or, slt*

 

1. Read registers *rs* and *rt*
2. Feed them to ALU
3. Update register file

- **LOAD and STORE**


- *lw rt, rs, imm*
- *sw rt, rs, imm*

 

1. Read register *rs* (and *rt* for store)
2. Feed *rs* and *immed* to ALU
3. Move data between mem and reg

- **BRANCH:**


- *beq rs, rt, imm*

 

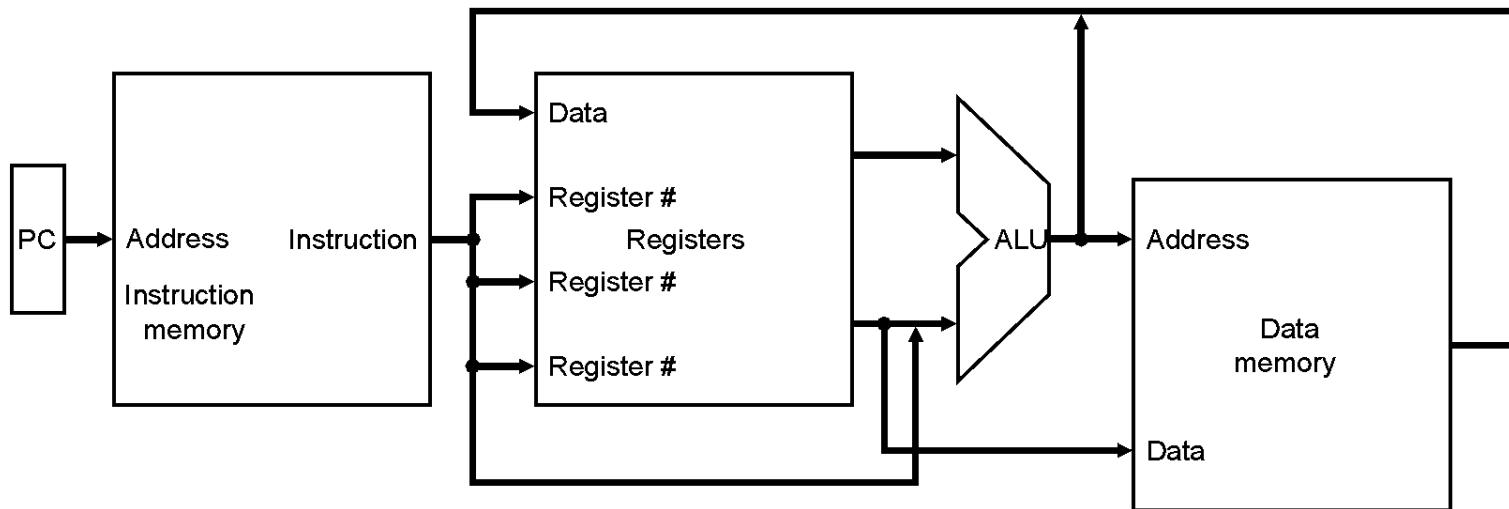1. Read registers *rs* and *rt*
2. Feed to ALU to compare
3. Add PC to disp; update PC


Processor Design

- **Generic Implementation:**
 - all instructions read some registers
 - all instructions use the ALU after reading registers
 - memory accessed & registers updated after ALU
- **Suggests basic design:**




R-Format Instructions

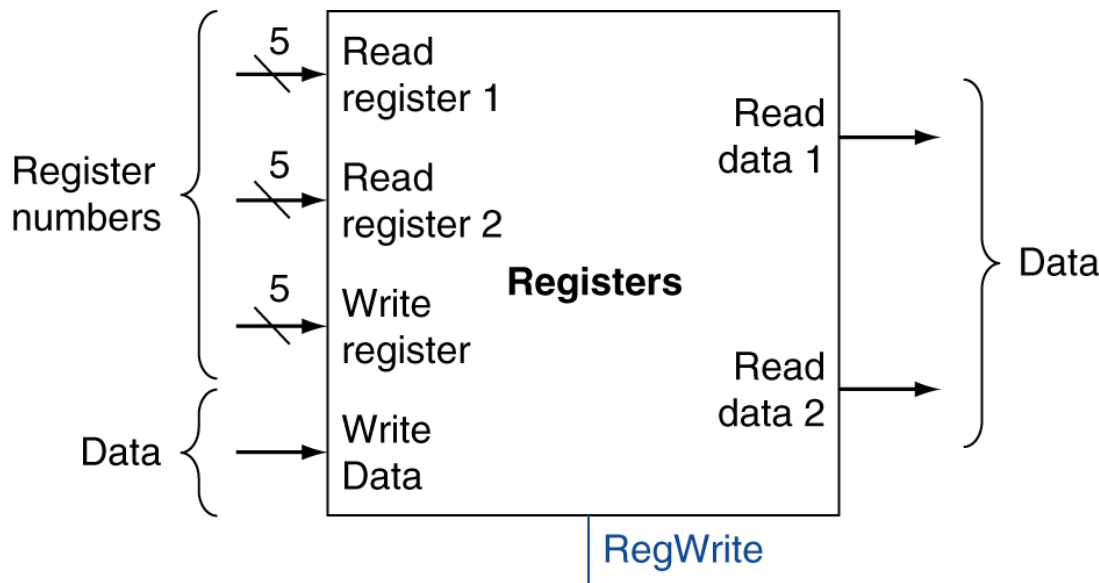- Read two register operands
- Perform arithmetic/logical operation
- Write register result





a. Registers

 

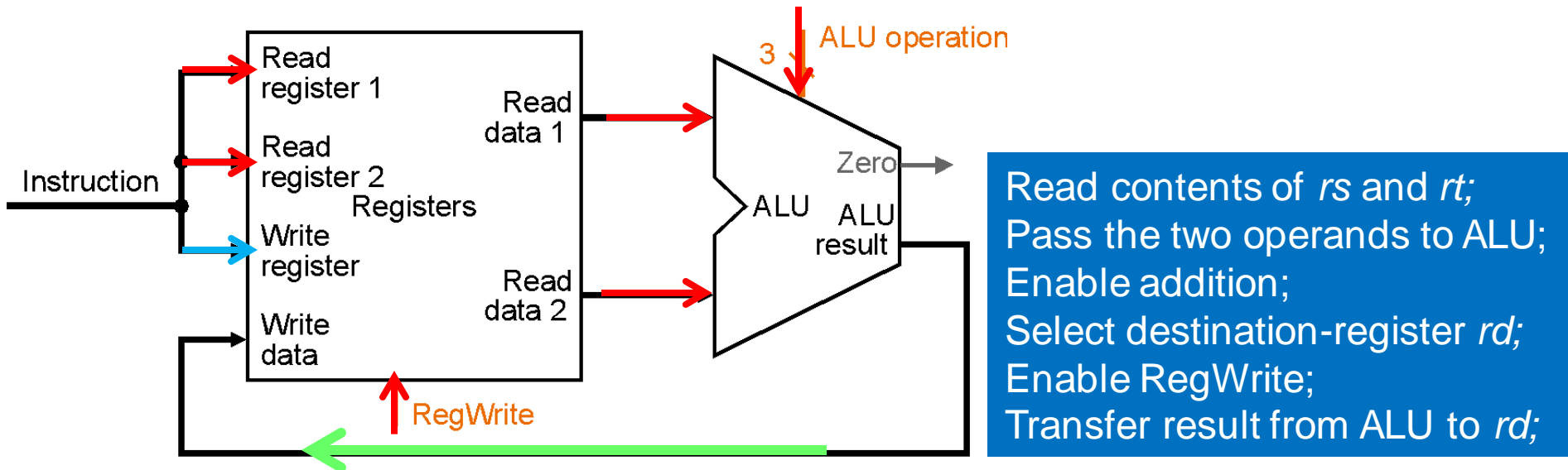 b. ALU


Datapath for Reg-Reg Operations

- $R[rd] \leftarrow R[rs] \text{ op } R[rt]$ Example: *add rd, rs, rt*
 - ID's of three registers obtained from *rs*, *rt*, and *rd* fields of the instruction (two sources and one destination)
 - ALU-operation signal depends on *op* and *funct*




Load/Store Instructions

 - Read register operands
- Calculate address using 16-bit offset
 - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory





a. Data memory unit

 

  b. Sign extension unit

Datapath for Load Operations

$R[rt] \leftarrow \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$ Example: *lw rt, rs, imm16*



Datapath for Load Operations

$R[rt] \leftarrow \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$ Example: *lw rt, rs, imm16*

Read contents of *rs*

Pass (*rs*) and sign-ext (*imm*) to ALU;


Enable addition to compute address;

Select dest register *rt*

Enable MemRead



Read memory location pointed by the computed address;

Transfer data from Mem to *rt*;

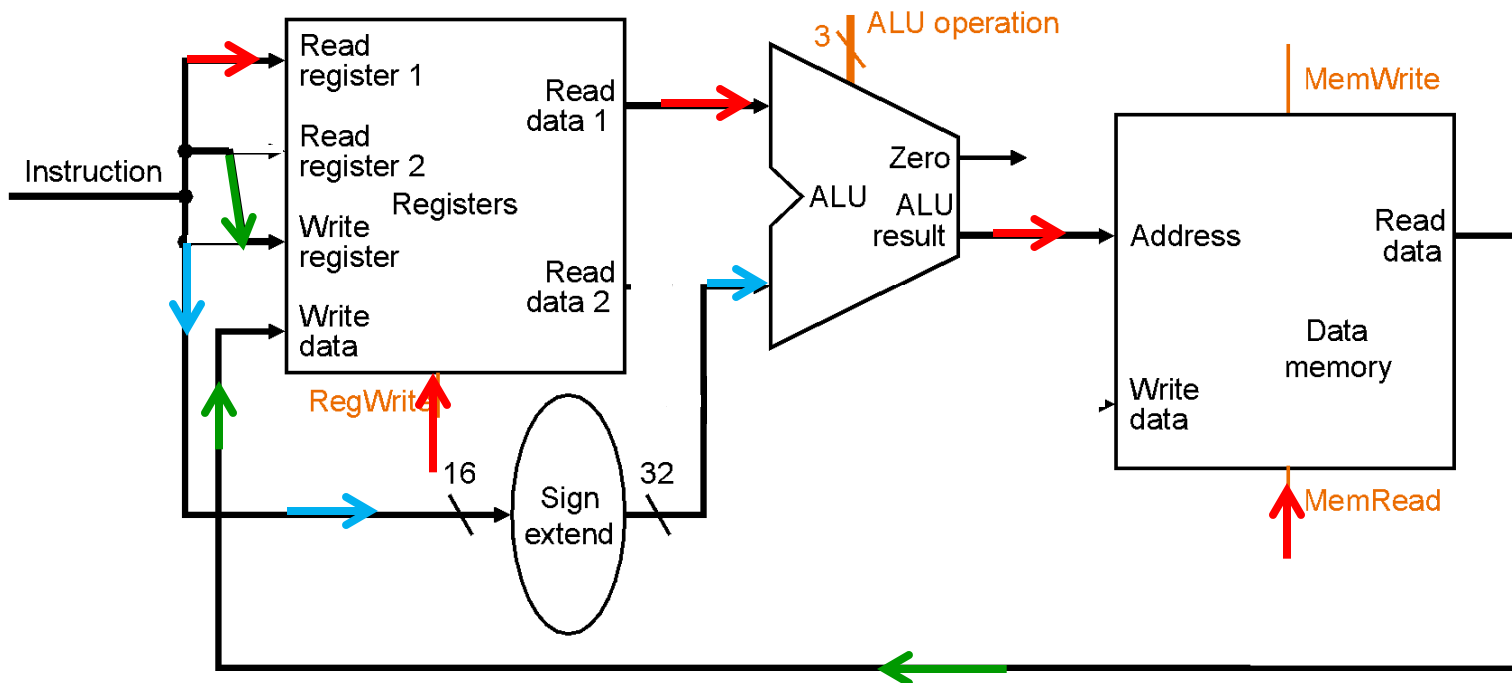

Datapath for Store Operations

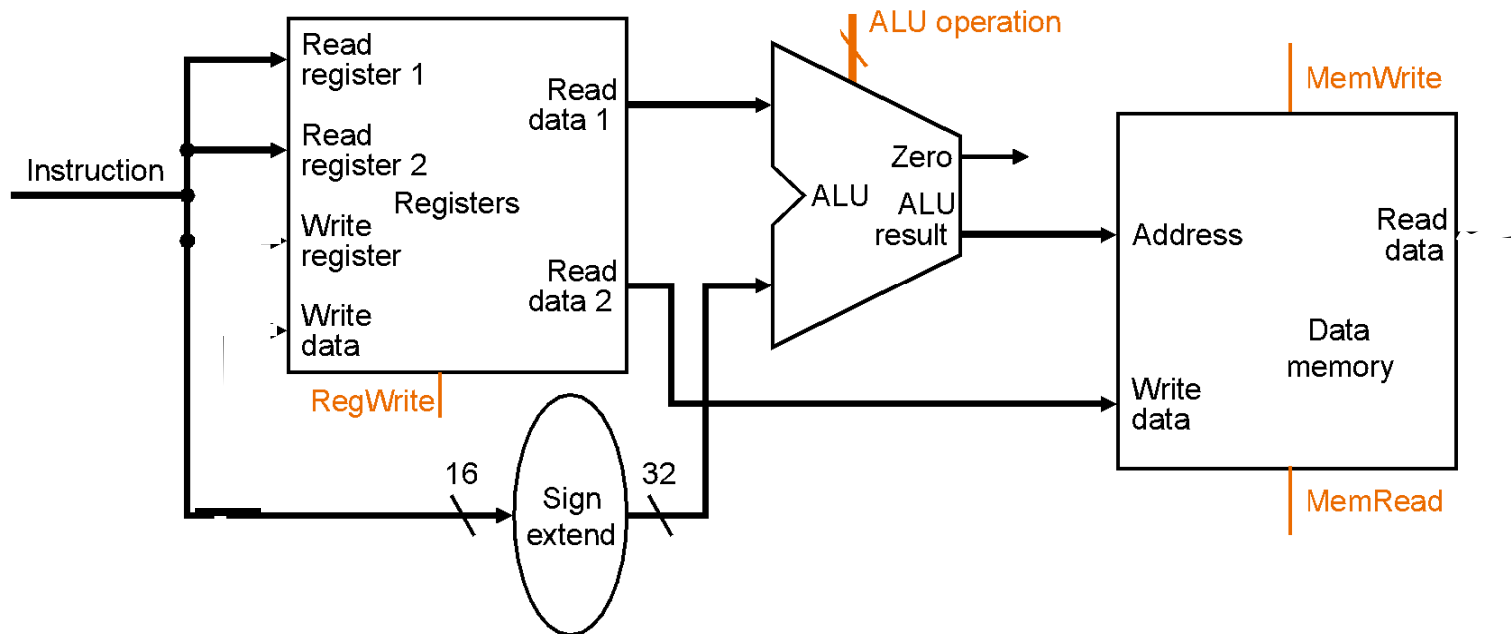 $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] \leftarrow \text{R}[\text{rt}]$ Example: `sw rt, rs, imm16`



Datapath for Store Operations

$\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] \leftarrow \text{R}[\text{rt}]$ Example: *sw rt, rs, imm16*

Read contents of *rs*


Pass (*rs*) and sign-ext (*imm*) to ALU;

Enable addition to compute address;

Select and read dest register *rt*


Enable MemWrite

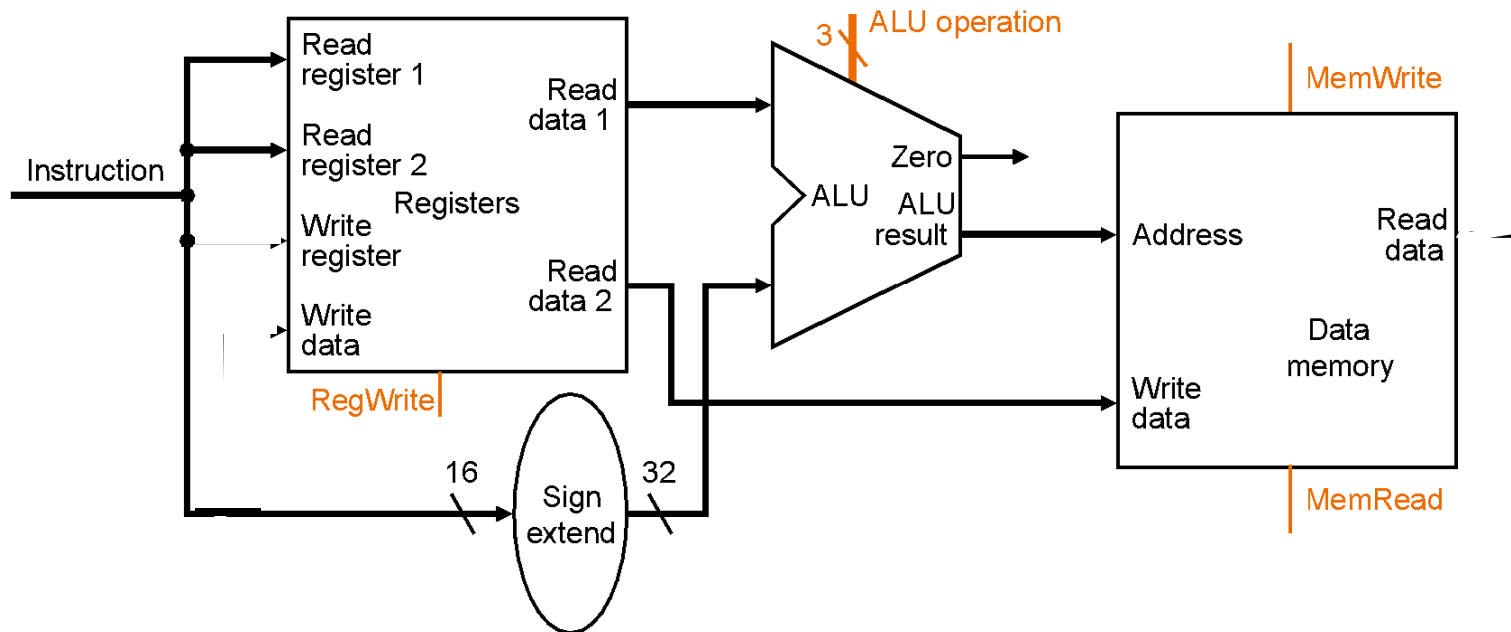Transfer (*rt*) to Mem location pointed by the computed address



Combining datapaths

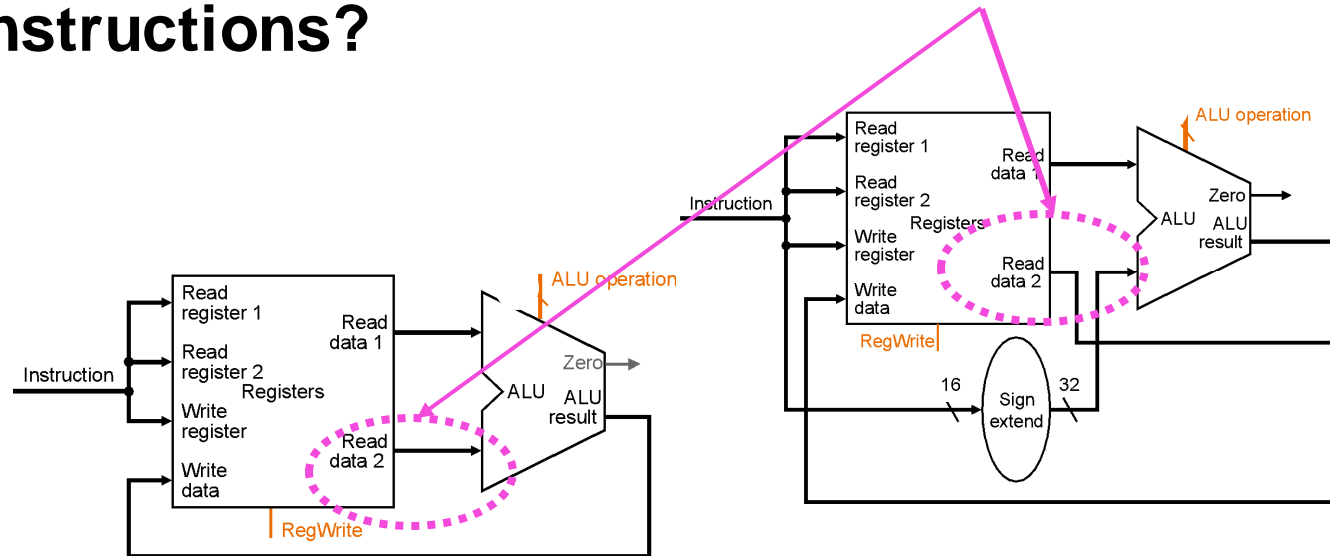- How do we allow different datapaths for different instructions?




R-type


Store

Combining datapaths

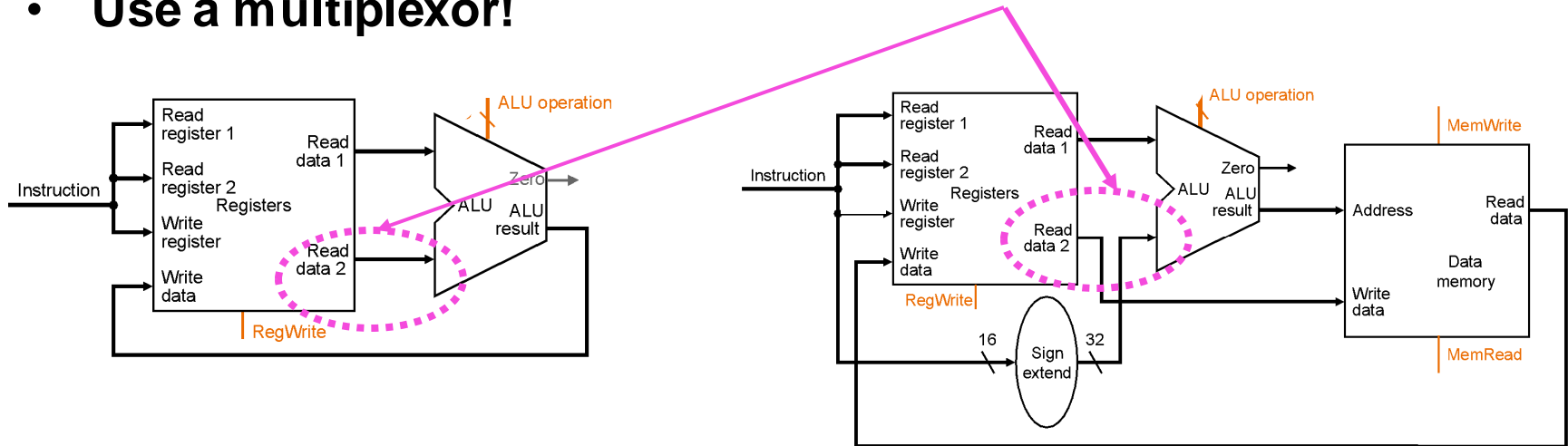- How do we allow different datapaths for different instructions?
- Use a multiplexor!



ALUscr (ALU second-input control)

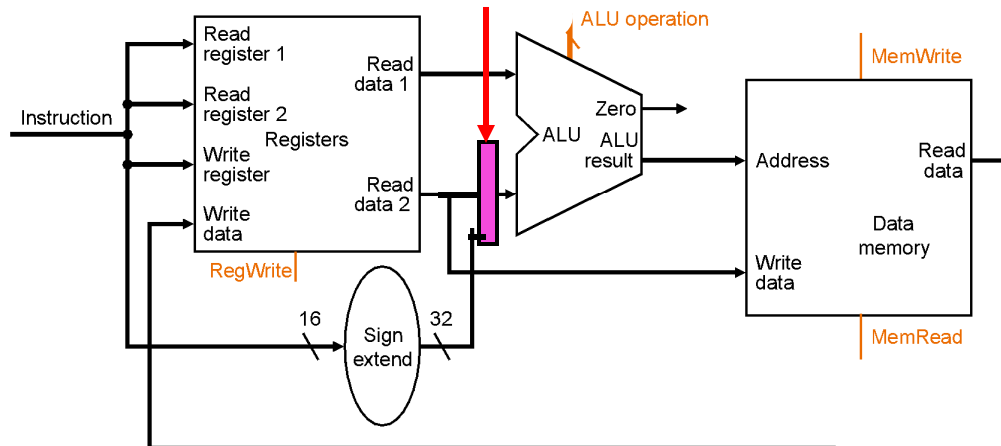



Branch Instructions

- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address
 - Sign-extend displacement
 - Shift left 2 places (word displacement)
 - Add to PC + 4
 - Already calculated by instruction fetch

Datapath for Branch Operations,,

beq rs, rt, imm16

We need to compare *rs* and *rt*

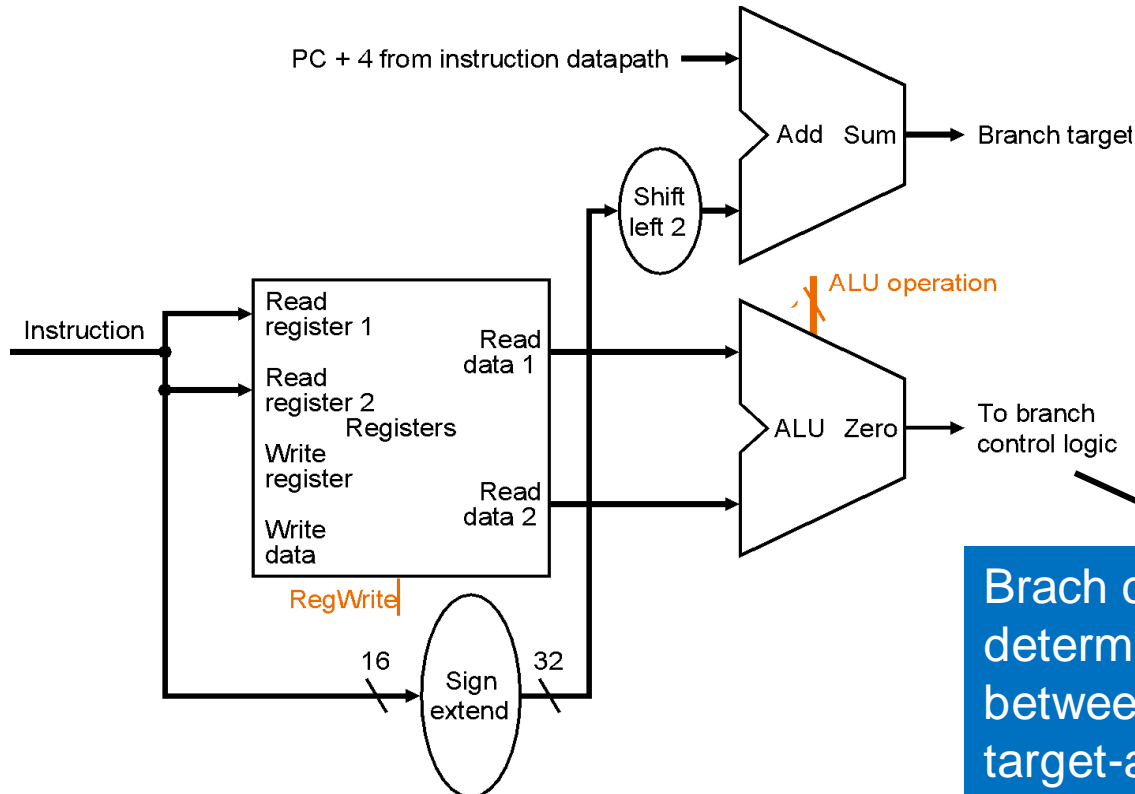
 


Datapath for Branch Operations


Read contents of *rs* and *rt*;
Compare them in ALU, by enabling ALU-op;
Read *imm* and sign-extend;
Shift-left by 2-bits to compute word-offset;
Add it with (PC+4) to compute target address;

beq rs, rt, imm16

We need to

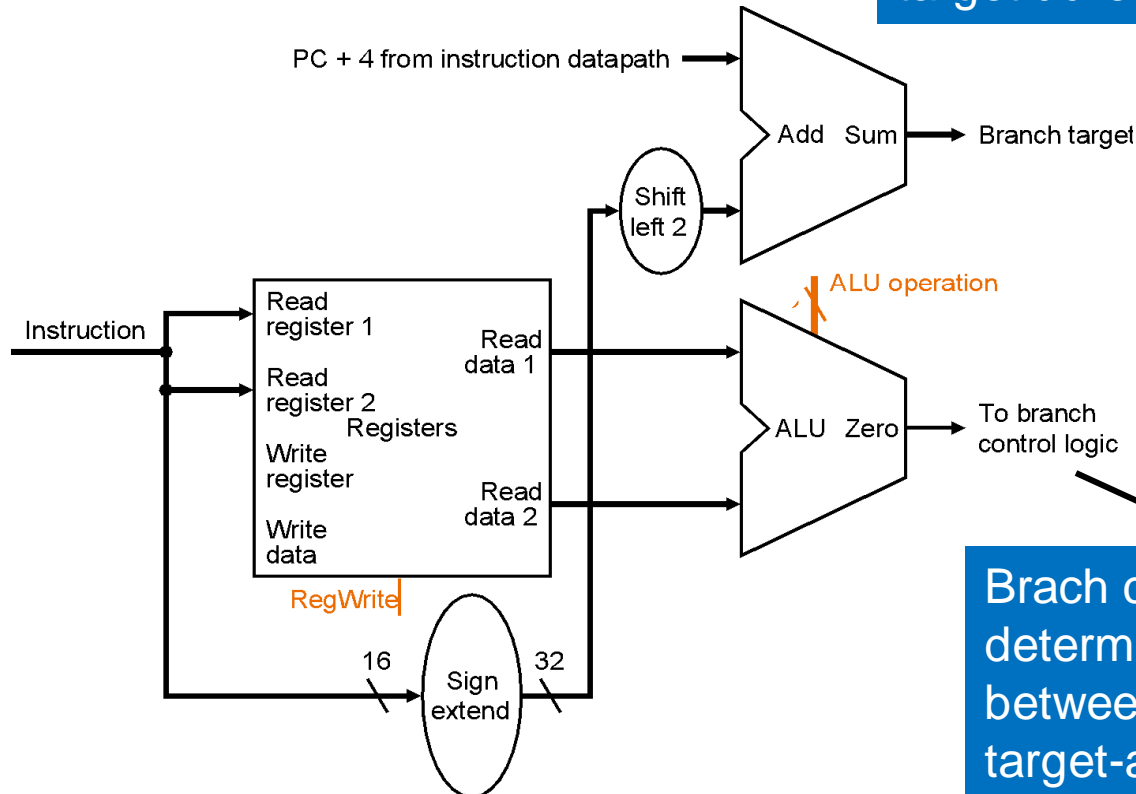 


Branch Instructions

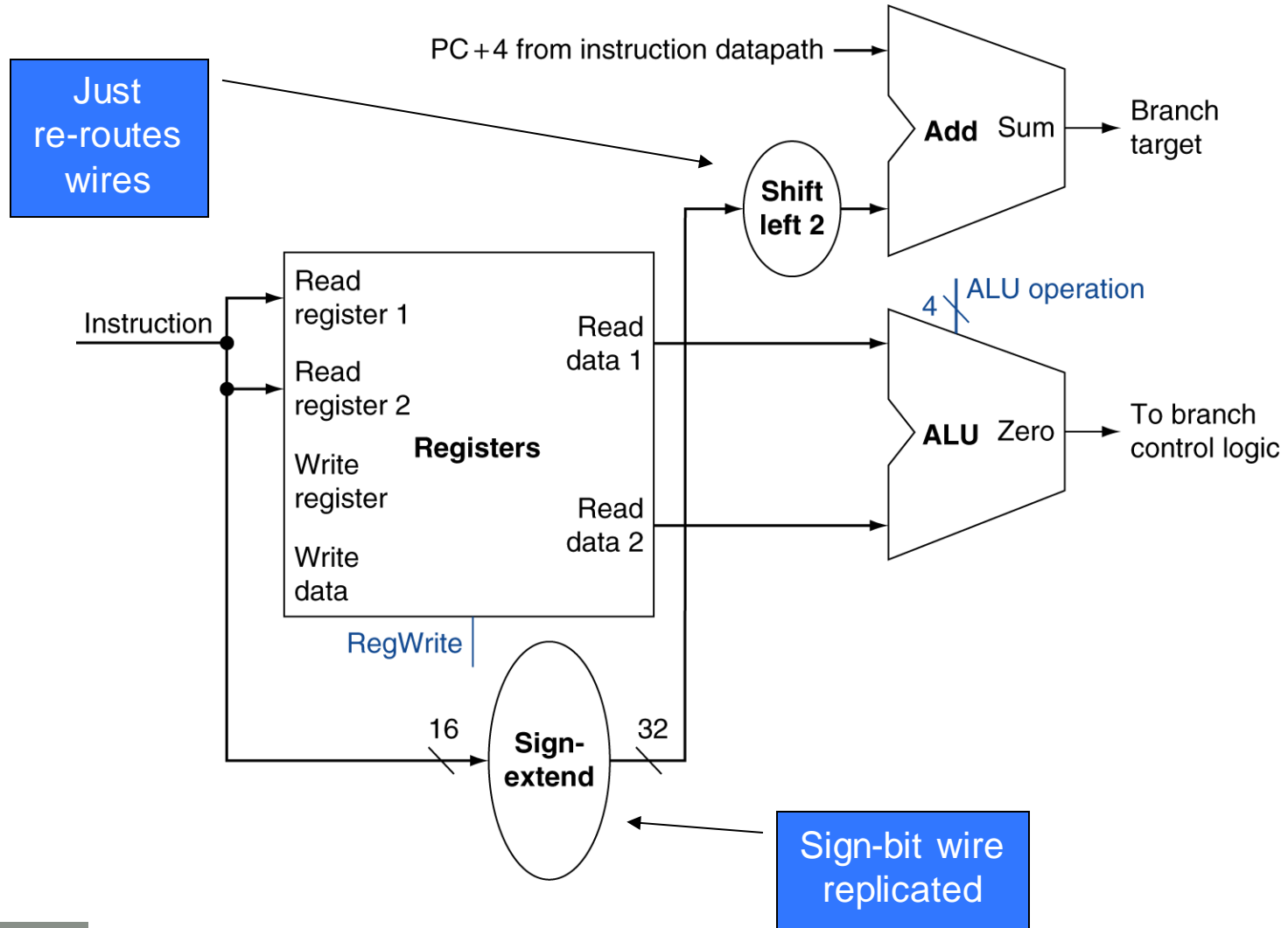


Composing the Elements

- First-cut data path does an instruction in one clock cycle
 - Each datapath element can only do one function at a time
 - Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions


R-Type/Load/Store Datapath

 


Full Datapath

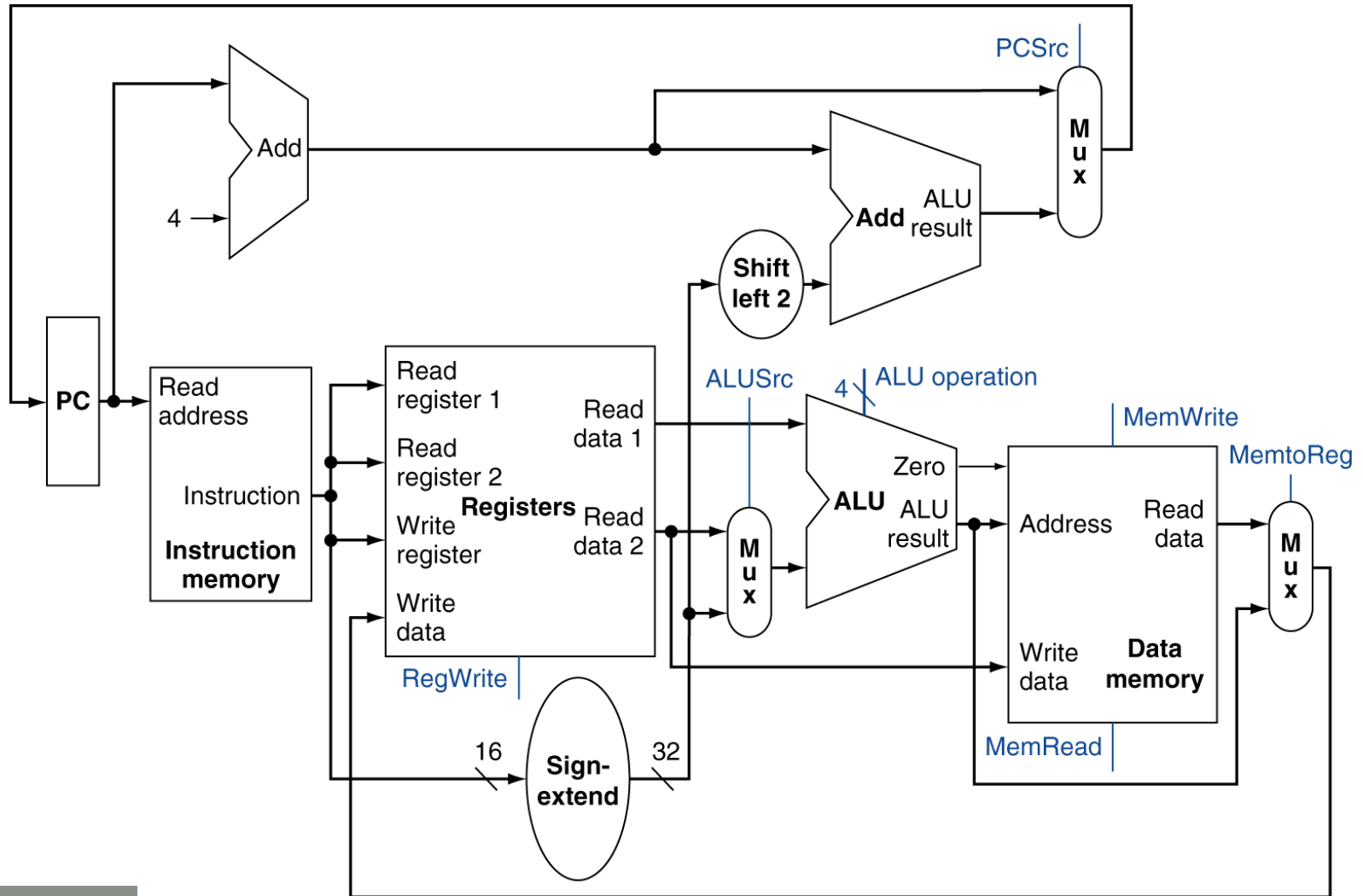

All together: the single cycle datapath

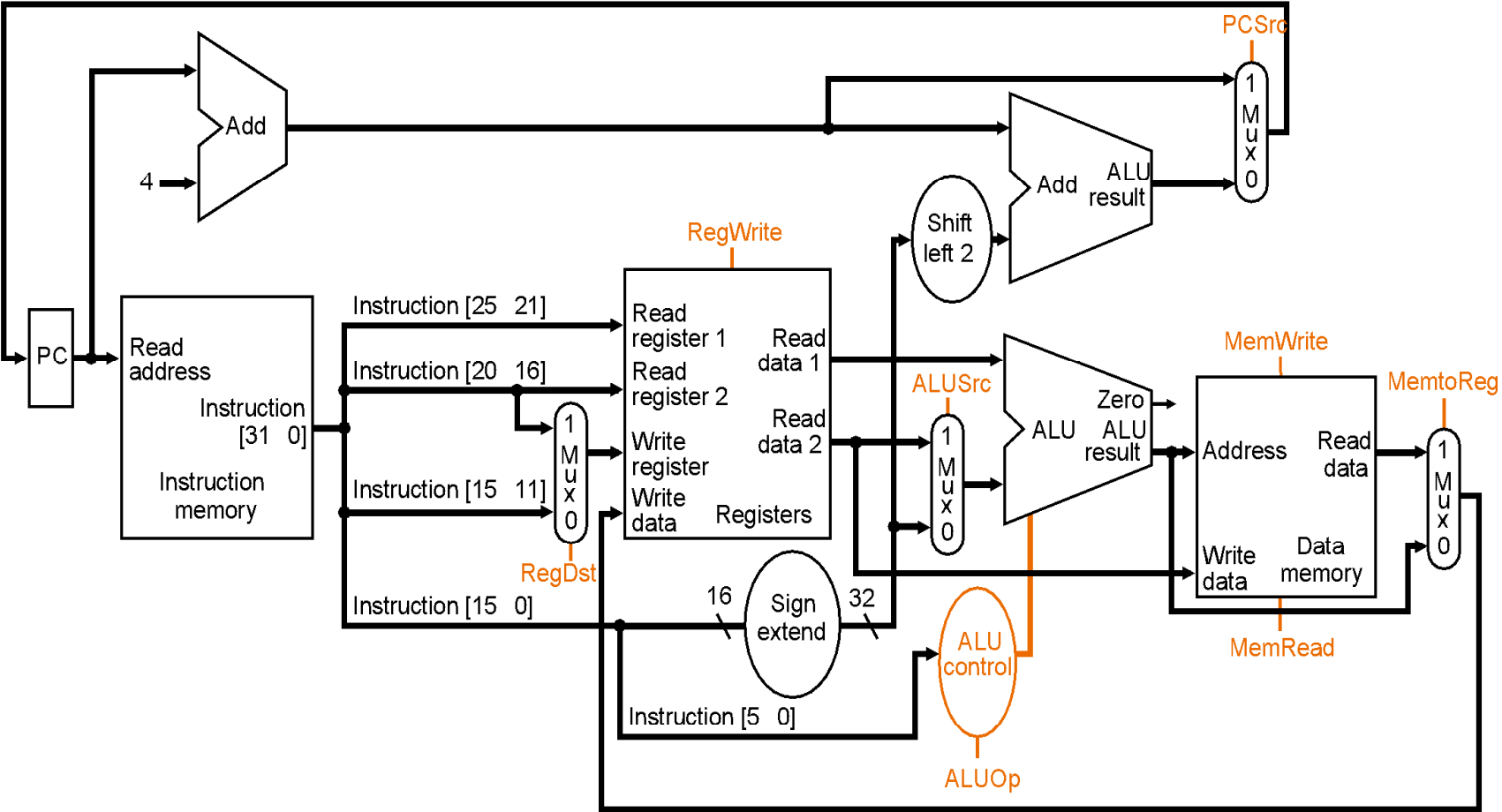


The R-Format (e.g. *add*) Datapath

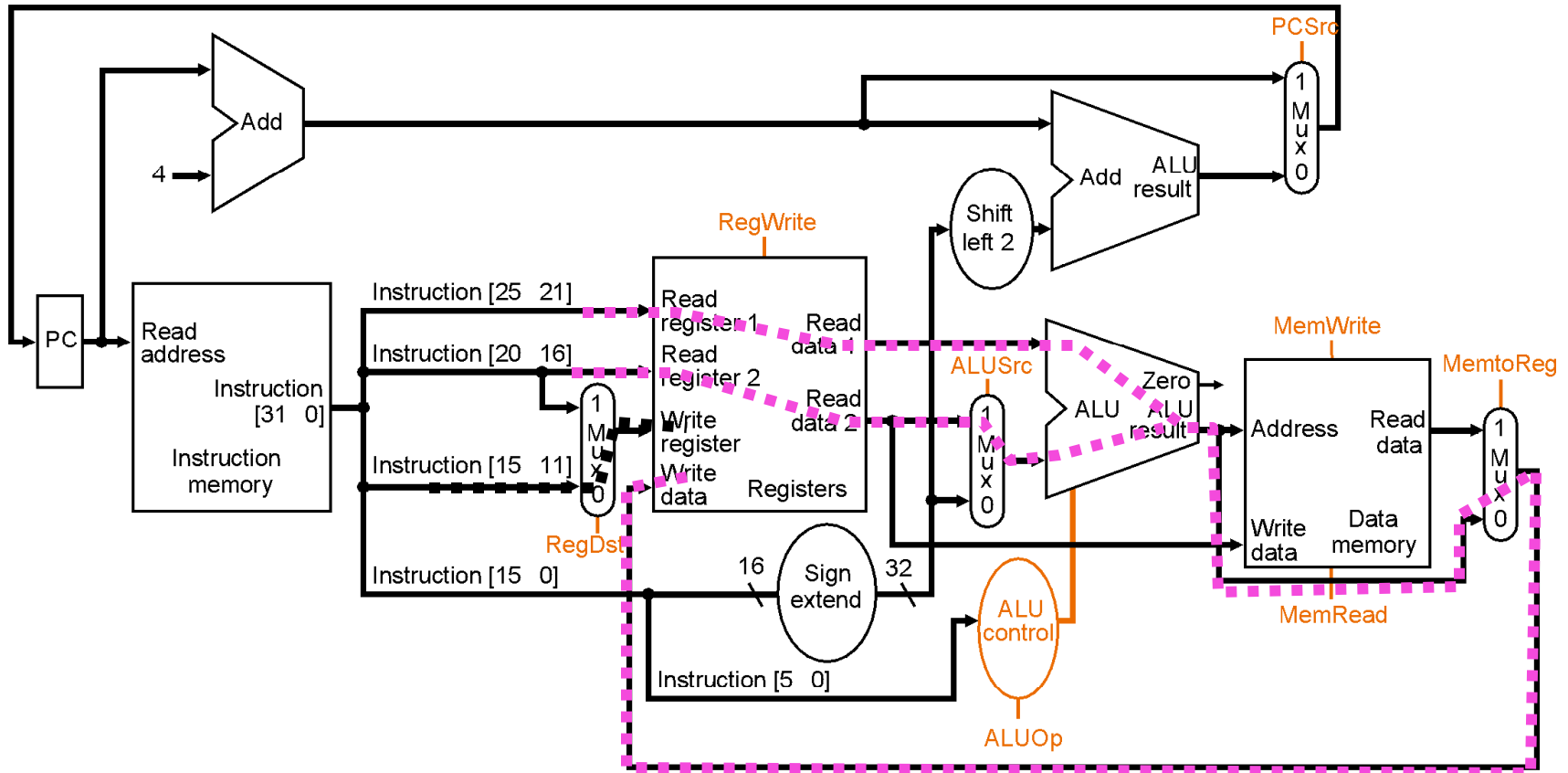


Need $ALUSrc=1$, $ALUOp="add"$, $MemWrite=0$, $MemToReg=0$,
 $RegDst = 0$, $RegWrite=1$ and $PCsrc=1$.

The Load Datapath

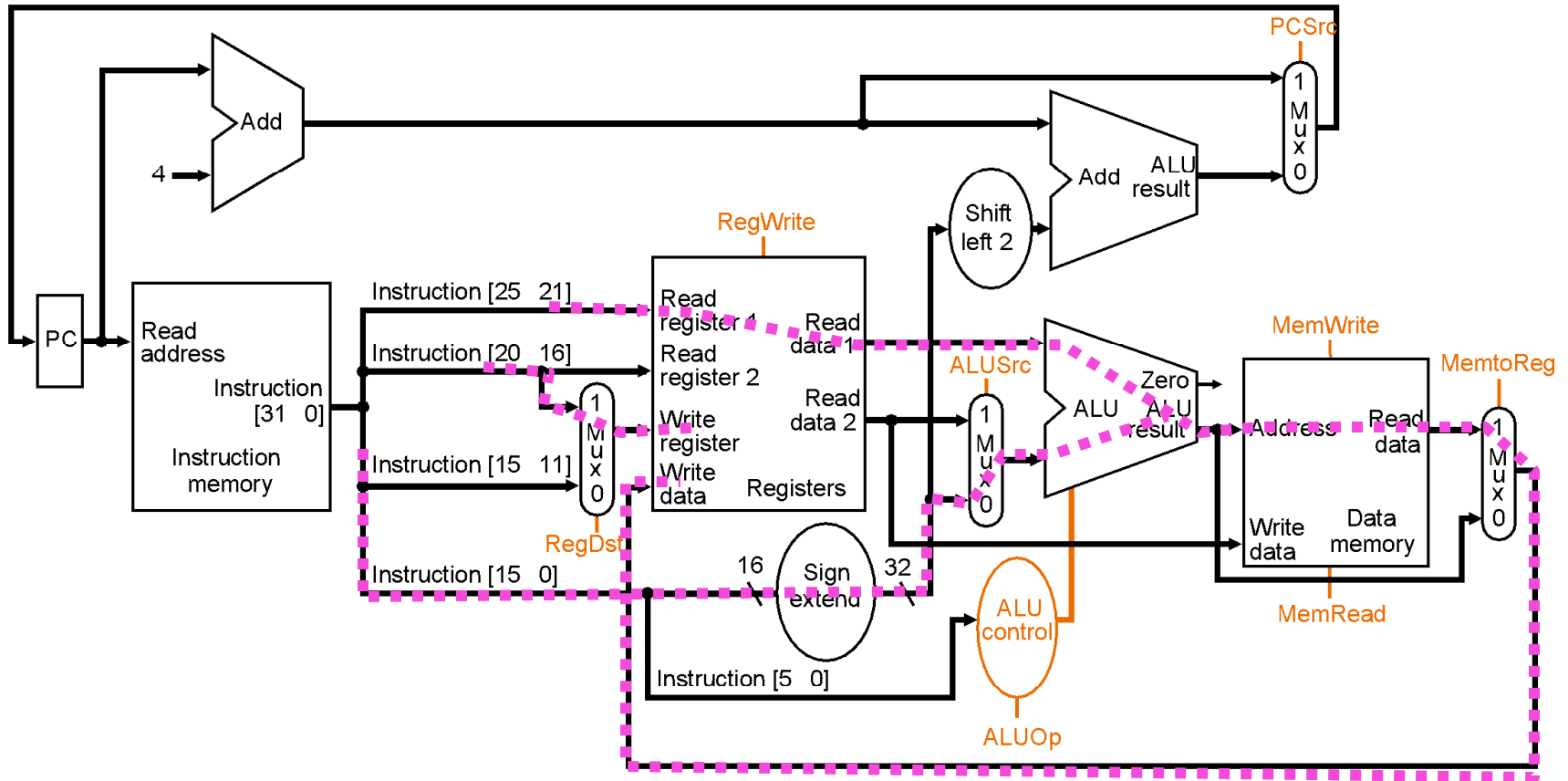


What control signals do we need for load??


The Store Datapath

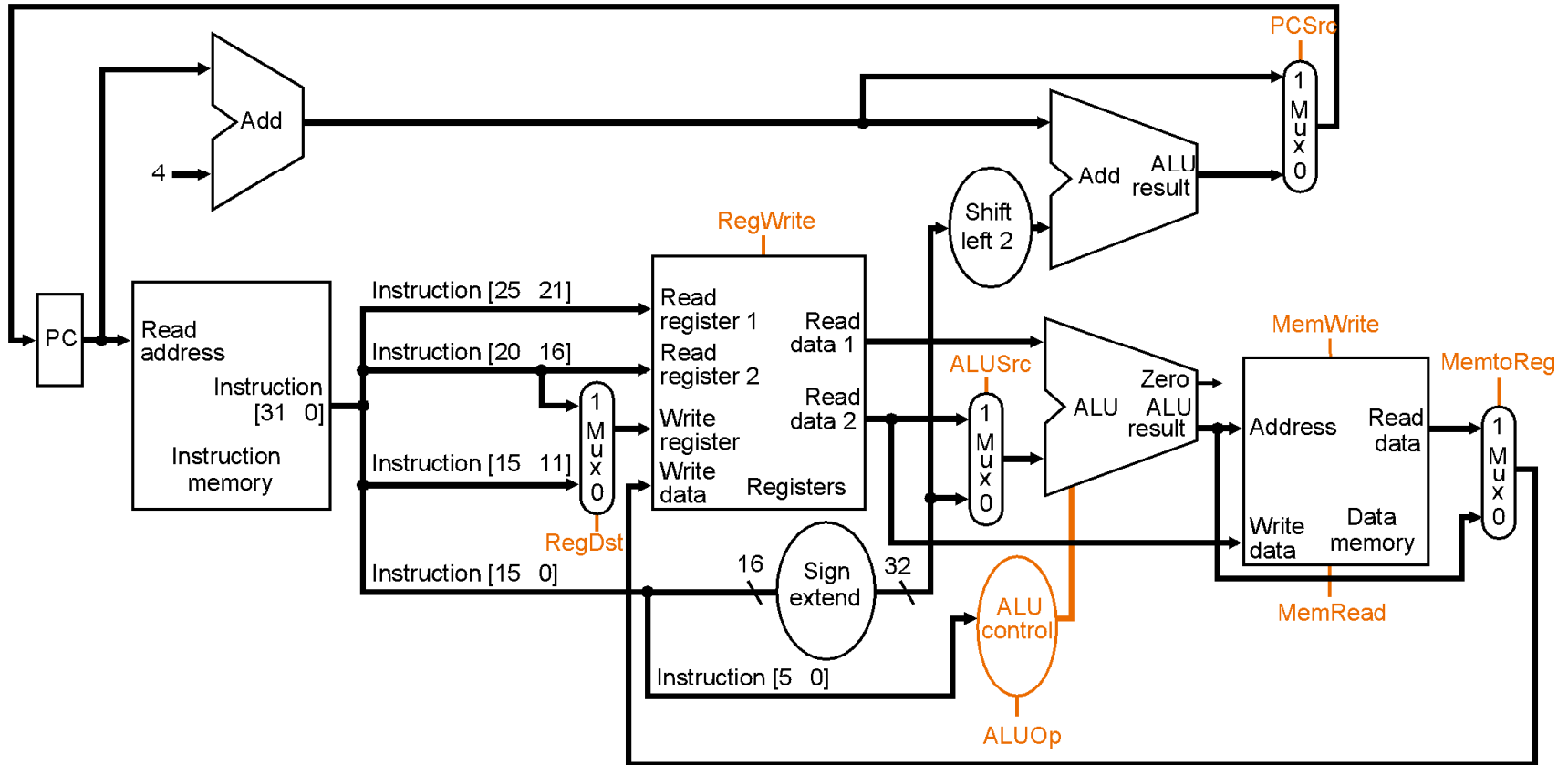

The beq Datapath

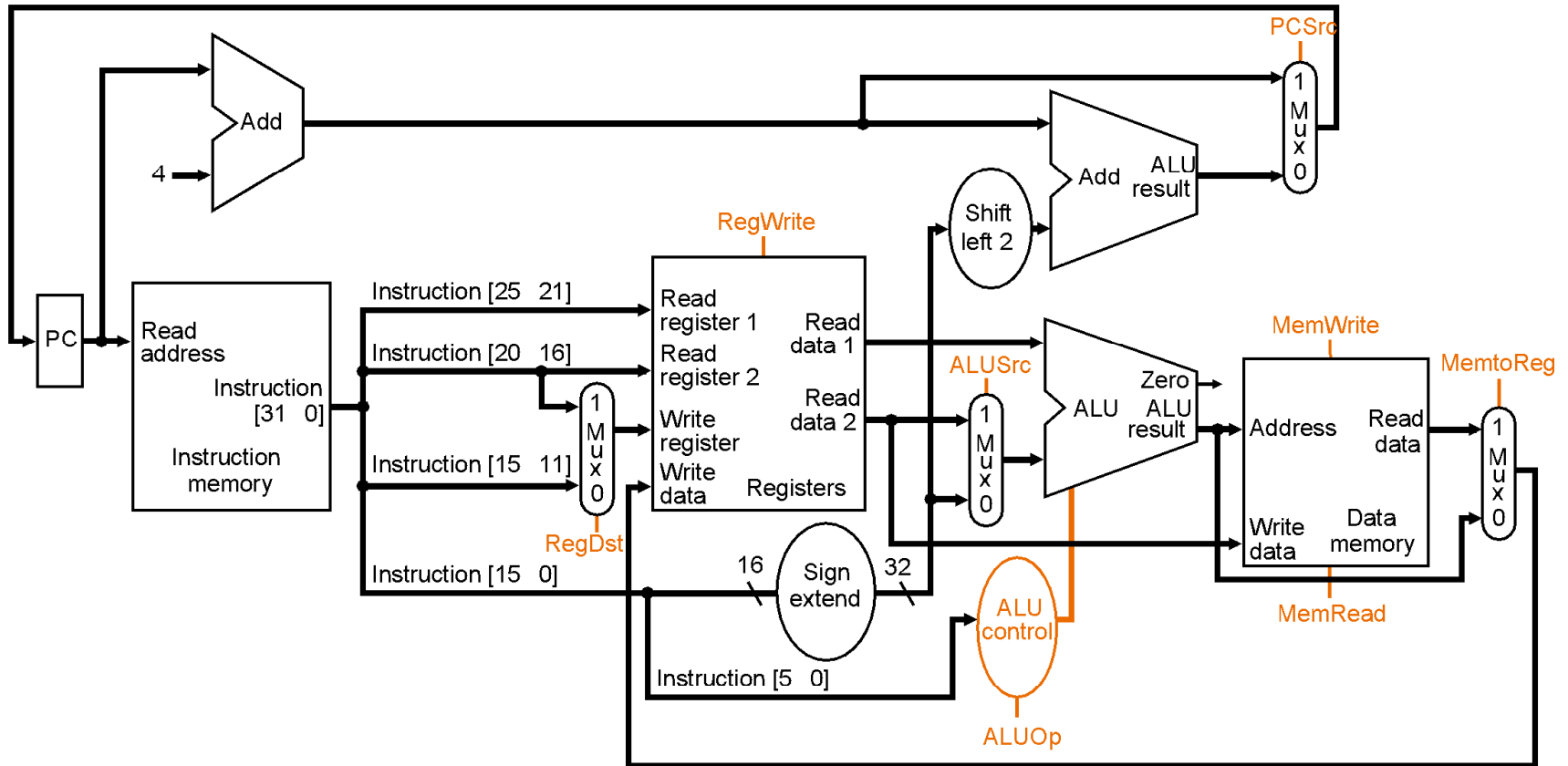

Control Signal Requirement

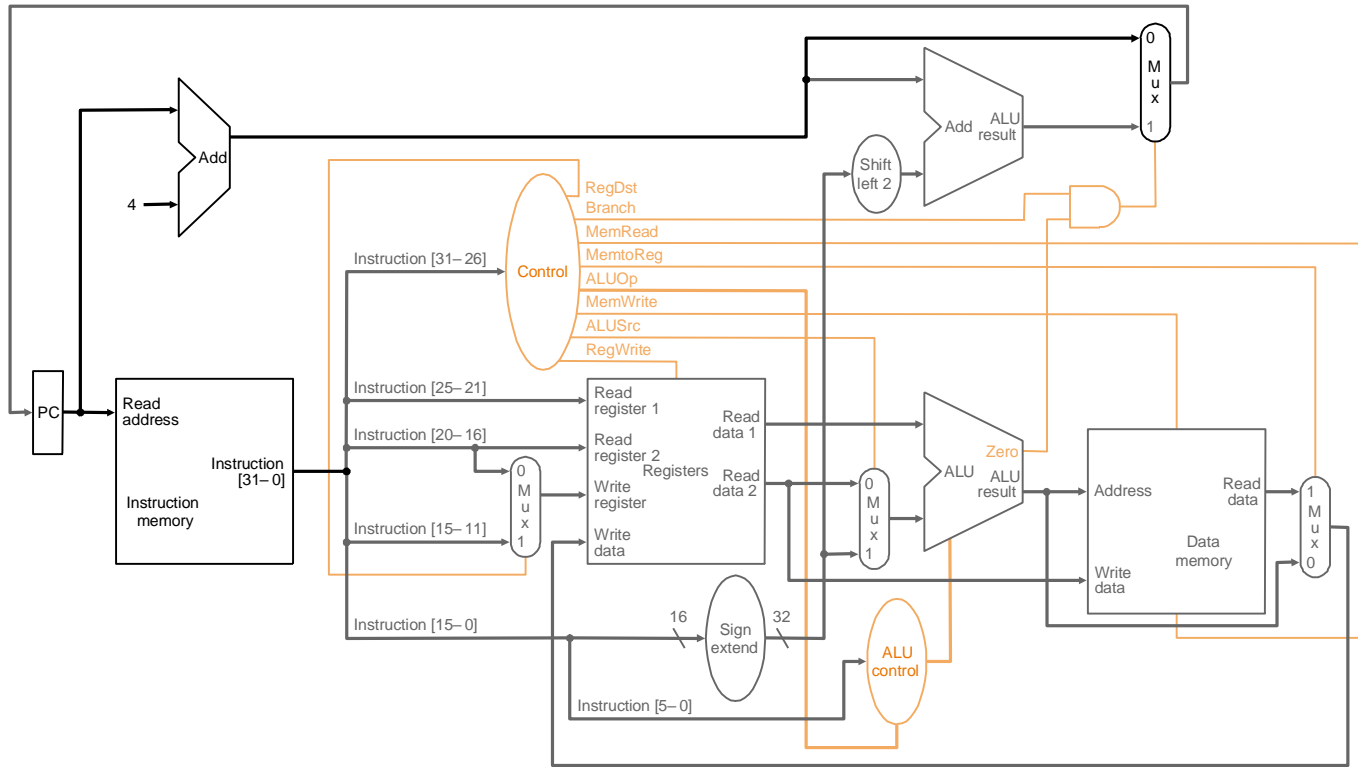

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

How to design the control unit?

- Input:
 - Op-code and function-field bits from instructions
- Output:
 - Desired control signals needed during the execution of an instruction
- For single-cycle implementation, the controller can be designed by a combinational circuit

Control

- Selecting the operations to perform (ALU, read/write, etc.)
- Controlling the flow of data (multiplexor inputs)
- Information comes from the 32 bits of the instruction
- Example:

add \$8, \$17, \$18


Instruction Format:

000000	10001	10010	01000	00000	100000
op	rs	rt	rd	shamt	funct

- ALU's operation based on instruction type and function code

ALU Control

 - ALU used for
 - Load/Store: $F = \text{add}$
 - Branch: $F = \text{subtract}$
 - R-type: F depends on funct field



ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR

ALU Control

- Assume 2-bit ALUOp derived from opcode
 - Combinational logic derives ALU control


opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111

Inputs to
control logic

outputs of
control logic



The Main Control Unit

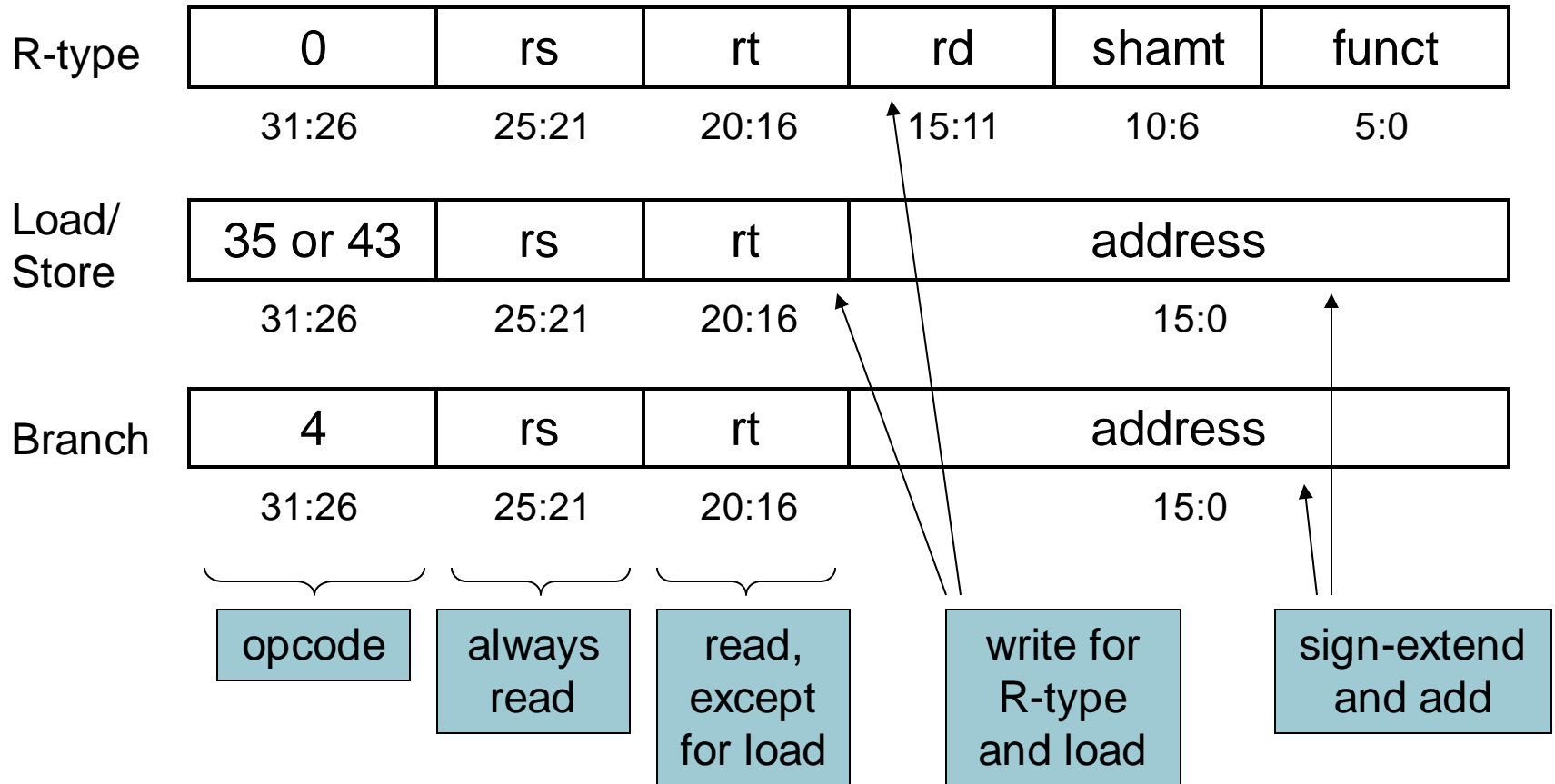■ Control signals derived from instruction




Control


- Simple combinational logic needed

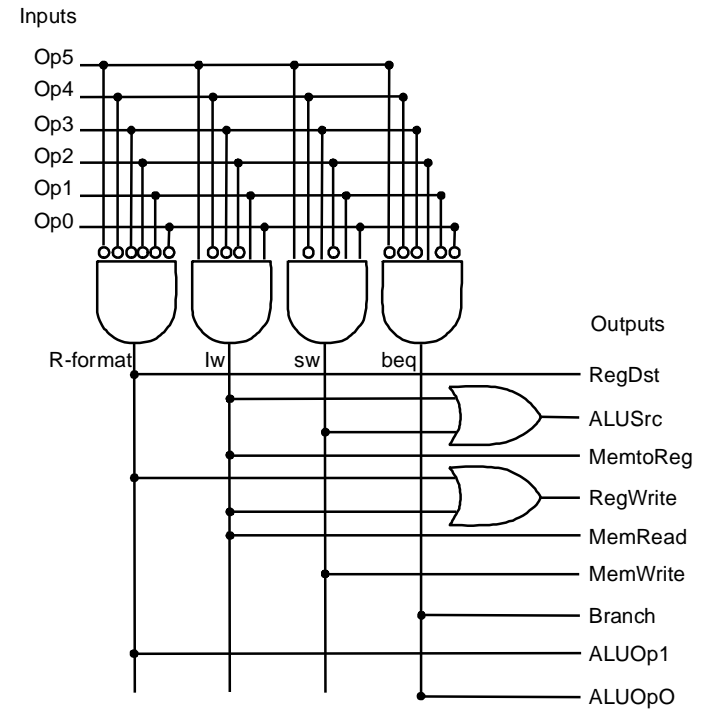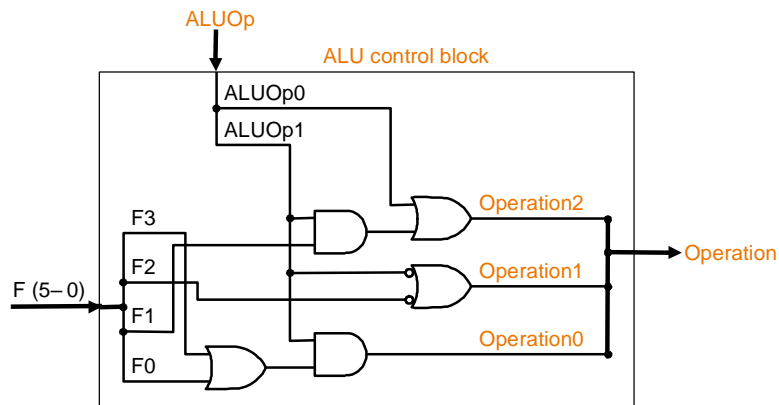


Datapath With Control

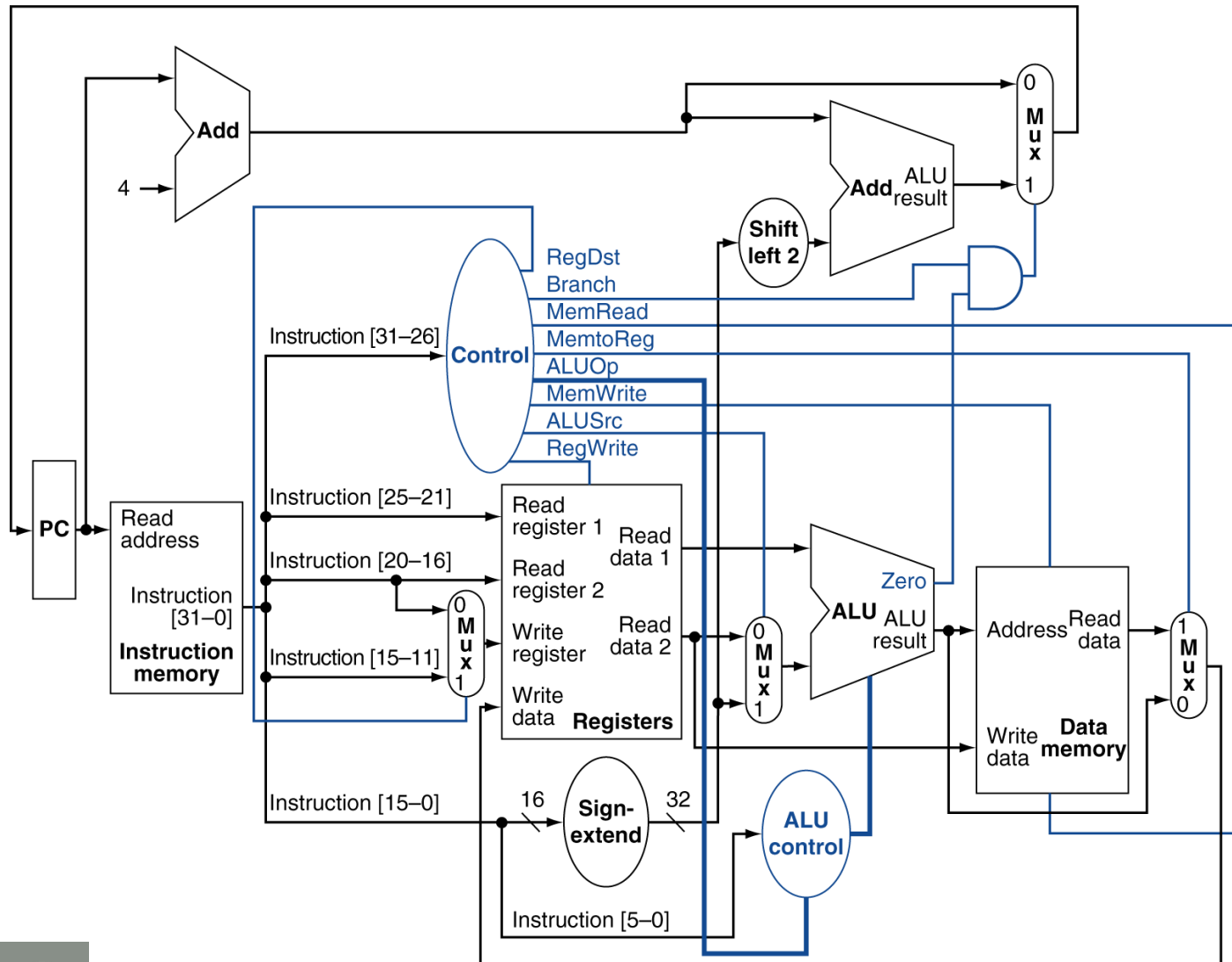


R-Type Instruction

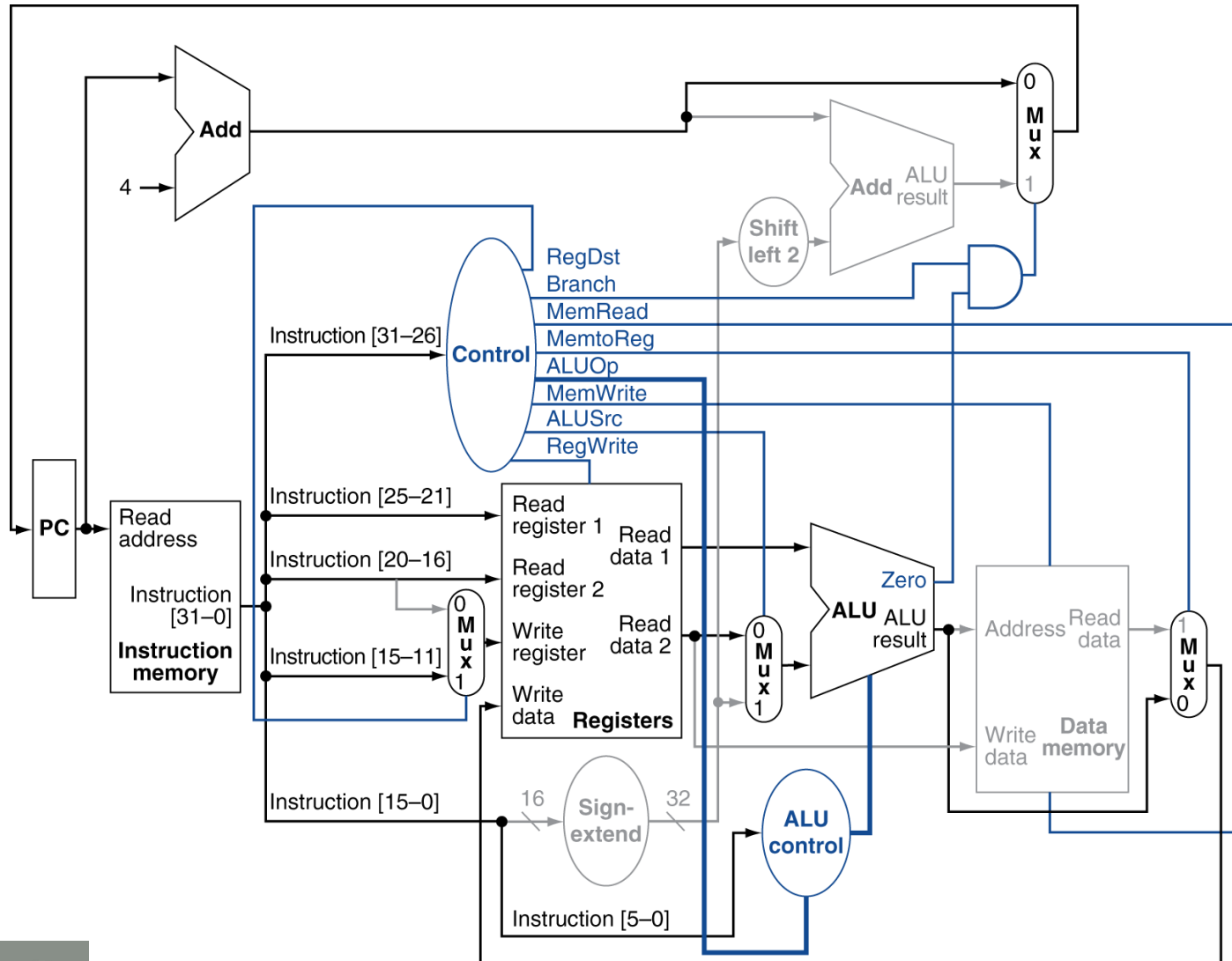


Load Instruction

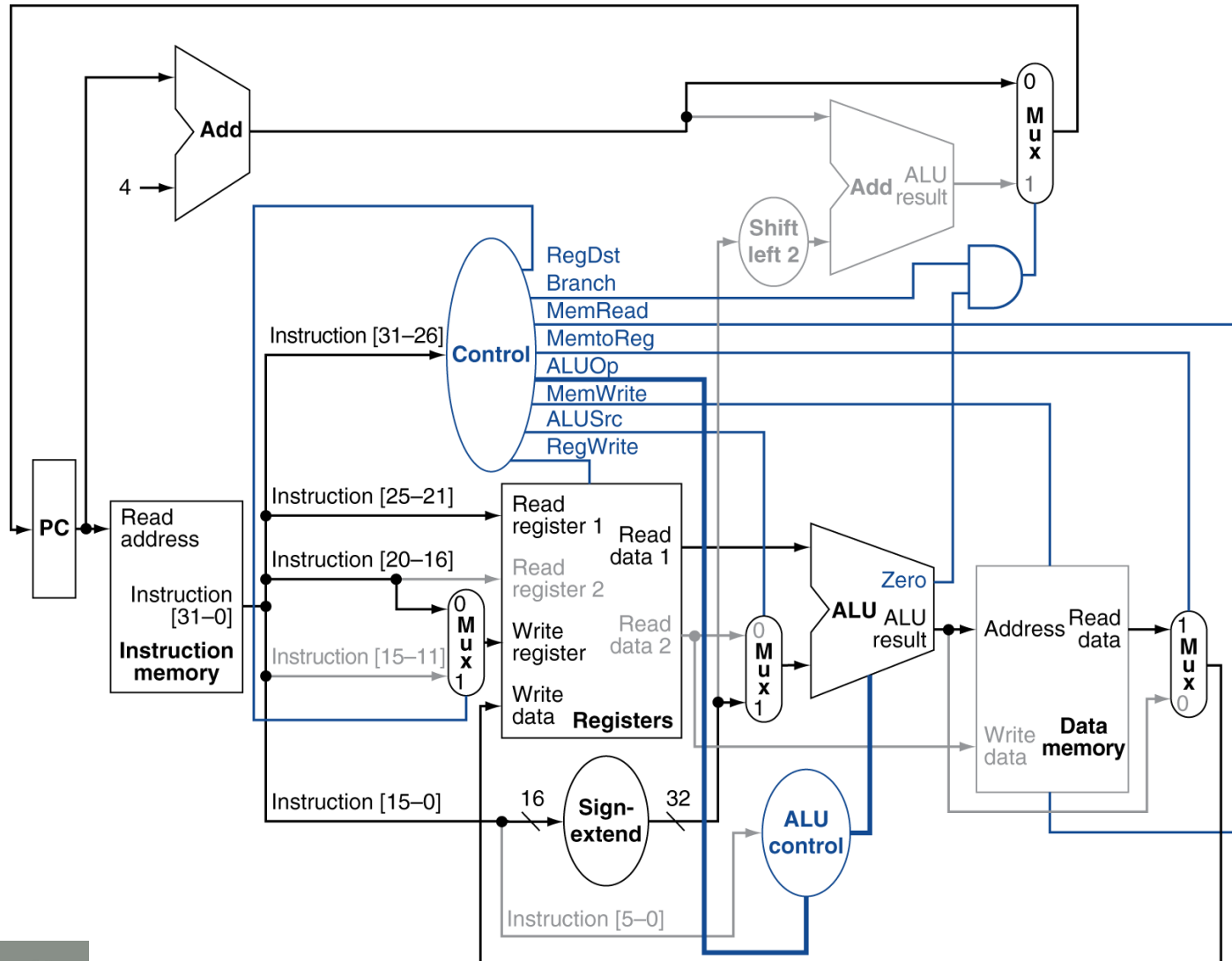

Branch-on-Equal Instruction

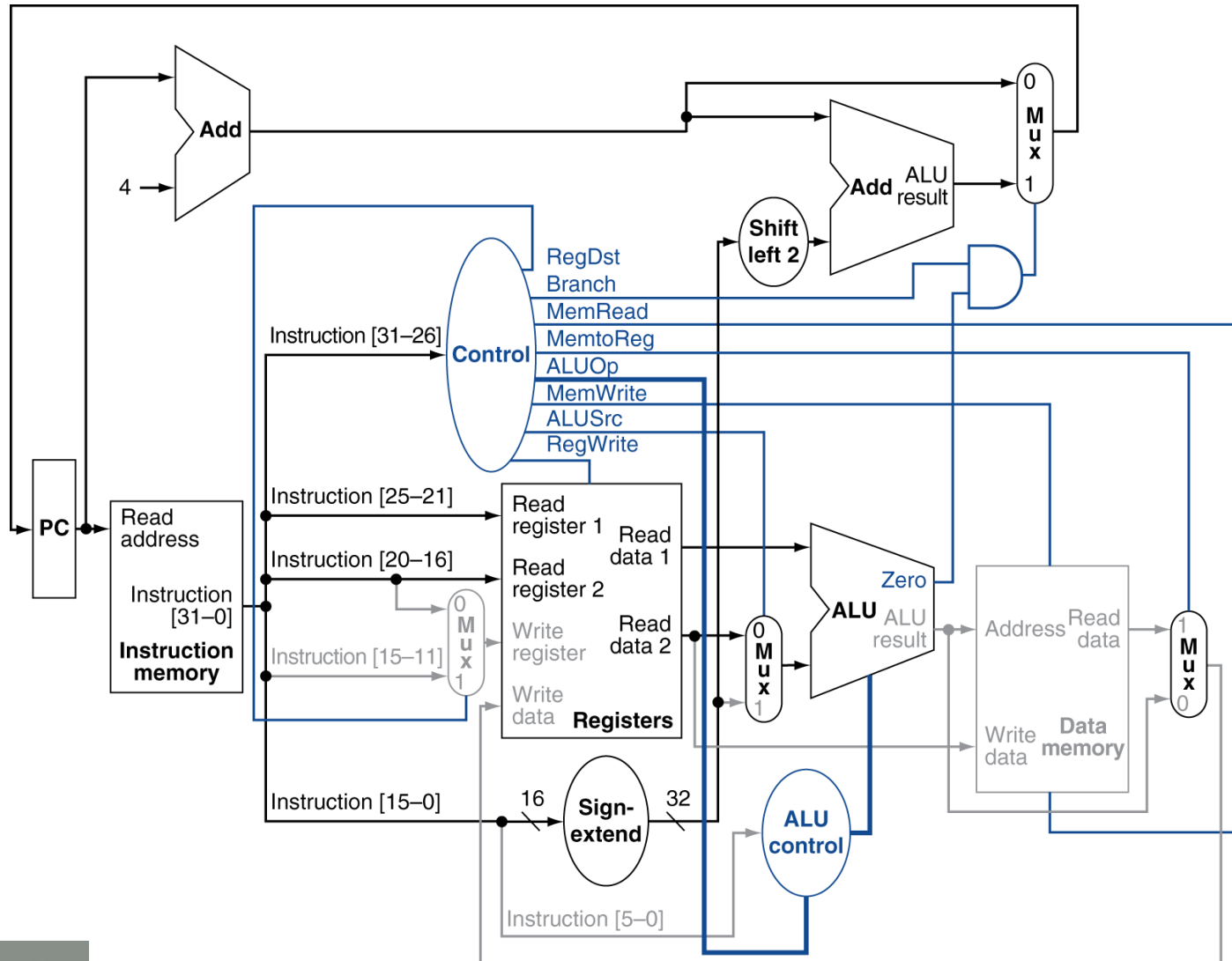


Implementing Jumps

 

- Jump uses word address
- Update PC with concatenation of
 - Top 4 bits of old PC
 - 26-bit jump address
 - Least significant two bits: 00
- Need an extra control signal decoded from op-code

Datapath with “Jumps” Added

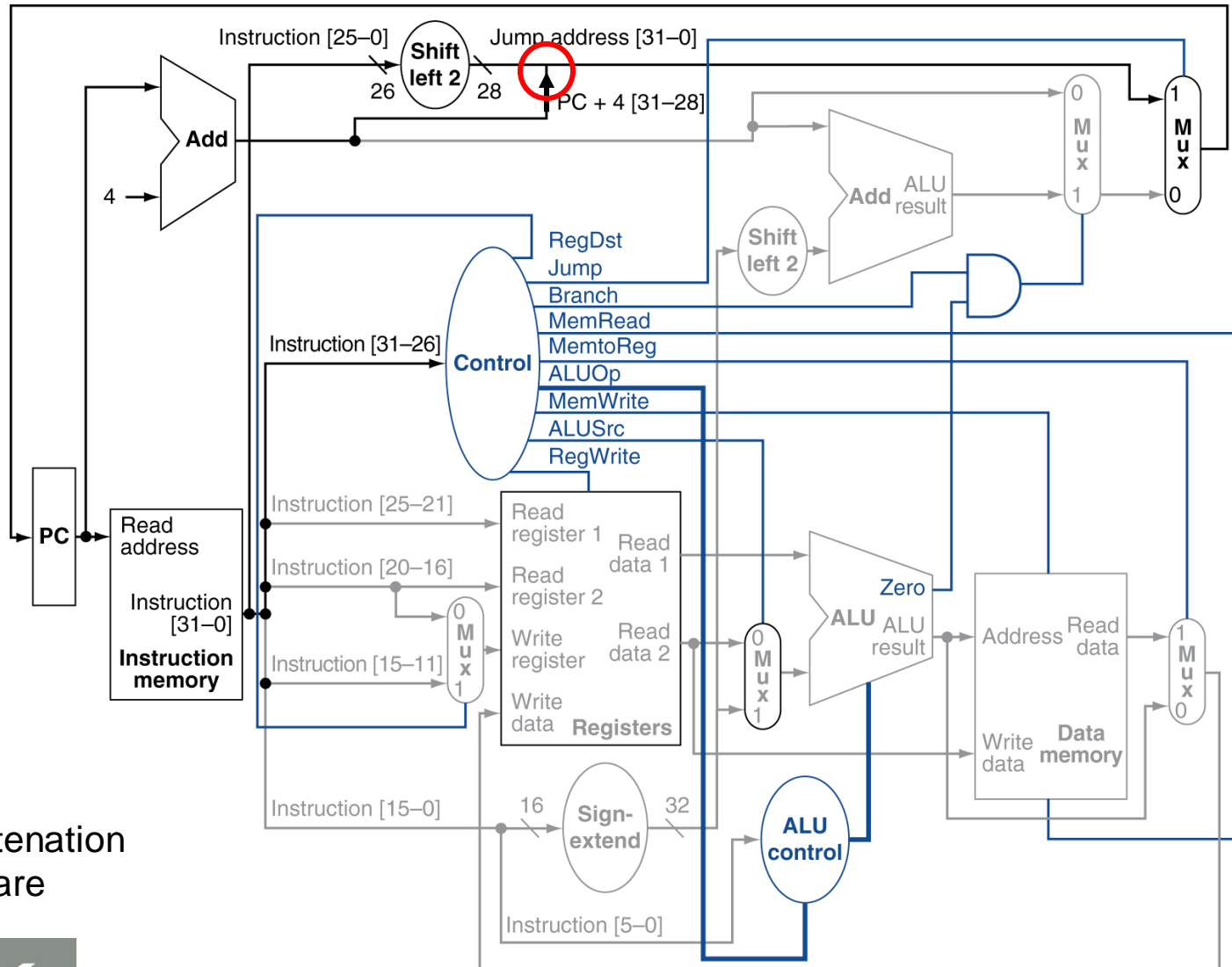

○ concatenation hardware

Performance Issues

- Longest delay determines clock period
 - Critical path: load instruction
 - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period for different instructions
- Violates design principle
 - Making the common case fast
- We will improve performance by pipelining

Key Points

- CPU is just a collection of state and combinational logic
- We have just designed a processor, at least in terms of functionality
- CPU time = $IC * CPI * CCT$
 - single-cycle machine degrades performance
 - Needs improved techniques such as pipelining

COA Tutorial – Processor Design

Lecture #29

30 September 2021

Processor Design

- Goal: To implement the MIPS “core” processor
 - load-store instructions: `lw, sw`
 - reg-reg instructions: `add, sub, and, or, slt`
 - control flow instructions: `beq`

Control lines (Bnegate Op1 Op0):

000 = and




001 = or

010 = add

110 = subtract

111 = slt

Implementing ALU

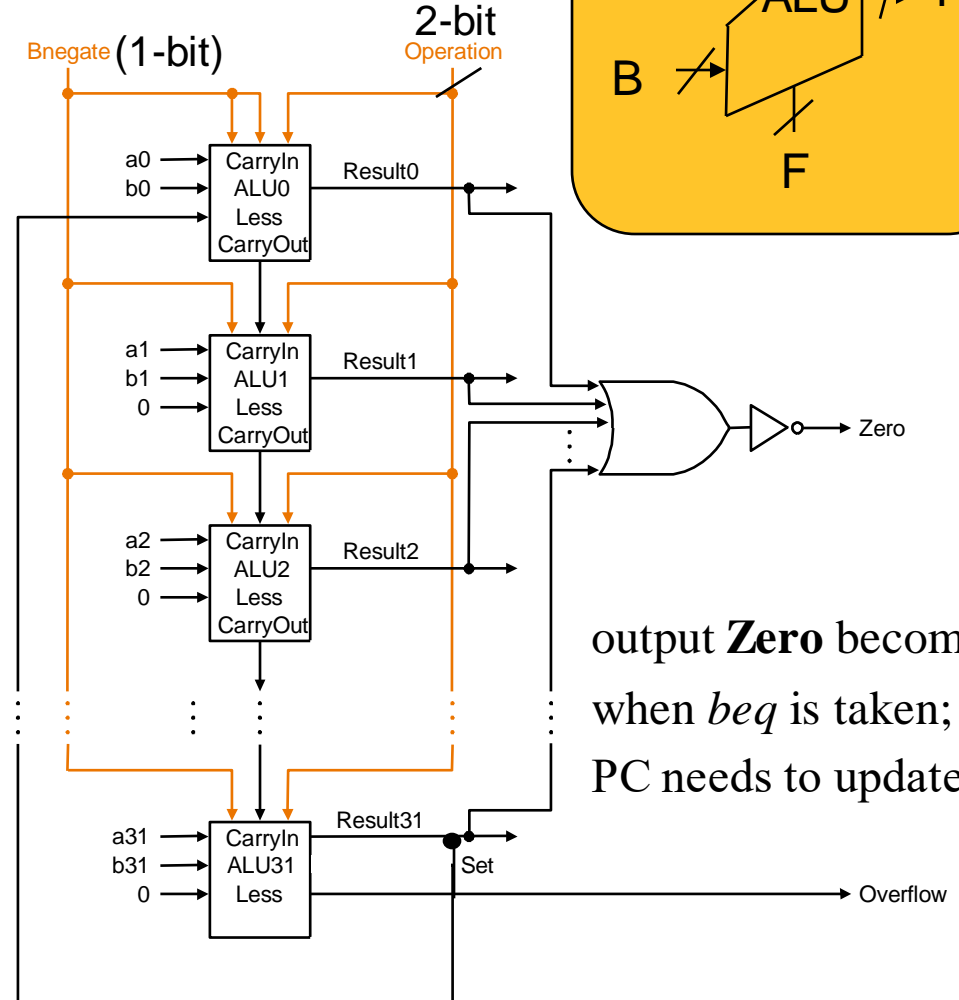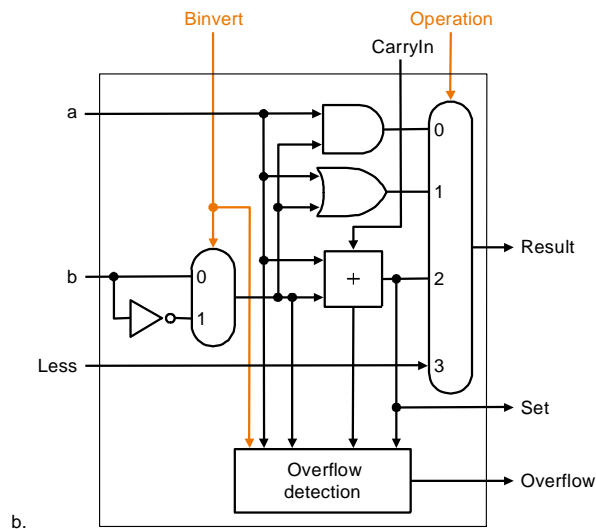 






output **Zero** becomes 1
when *beq* is taken;
PC needs to be updated ...

This ALU implements MIPS *add*, *sub*, *and*, *or*, *slt*, and *beq*

Simple Hardware Implementation of a CPU


- Functional units we need for implementing instructions

32-bit

     

Register File: Read

- Built using D flip-flops

 


add rd, rs, rt

MIPS has a 32×32 -bit register file
Use for frequently accessed data
Numbered 0 to 31

Assembler names


\$t0, \$t1, ..., \$t9 for temporary values

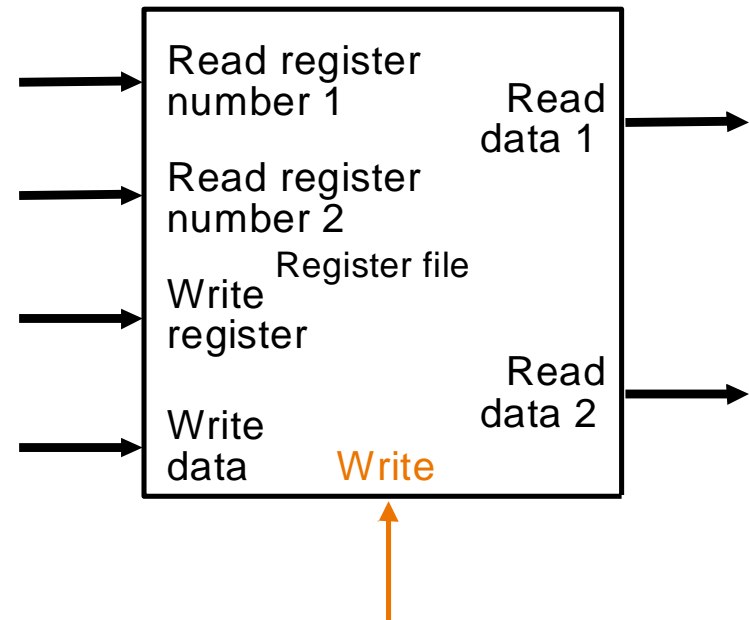\$s0, \$s1, ..., \$s7 for saved variables




Register File: Write

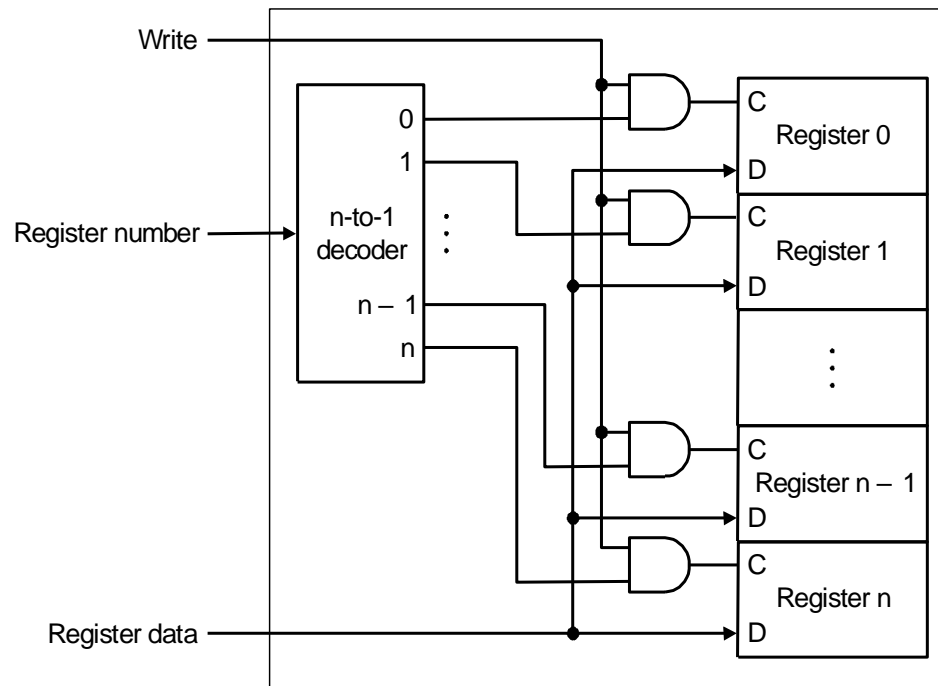- use the clock to determine when to write, provided *Write* is enabled



add rd, rs, rt

Control Signal Requirement

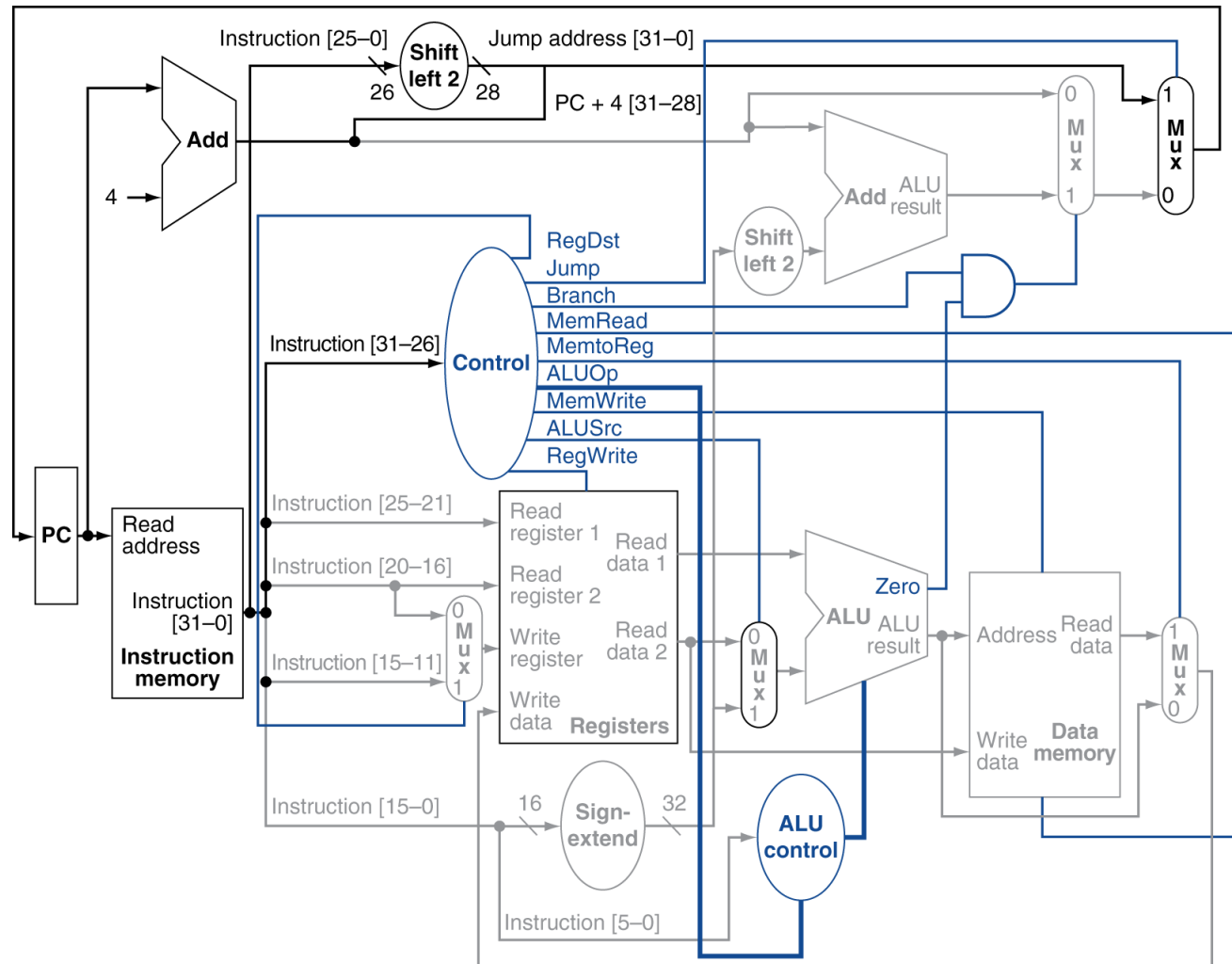


JUMP = 0

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUp0
R-format	1	0	0	1	0	0	0	ADD/SUB/Logical	
lw	0	1	1	1	1	0	0	ADD	
sw	X	1	X	0	0	1	0	ADD	
beq	X	0	X	0	0	0	1	SUB	

Logic Faults in MIPS Processor

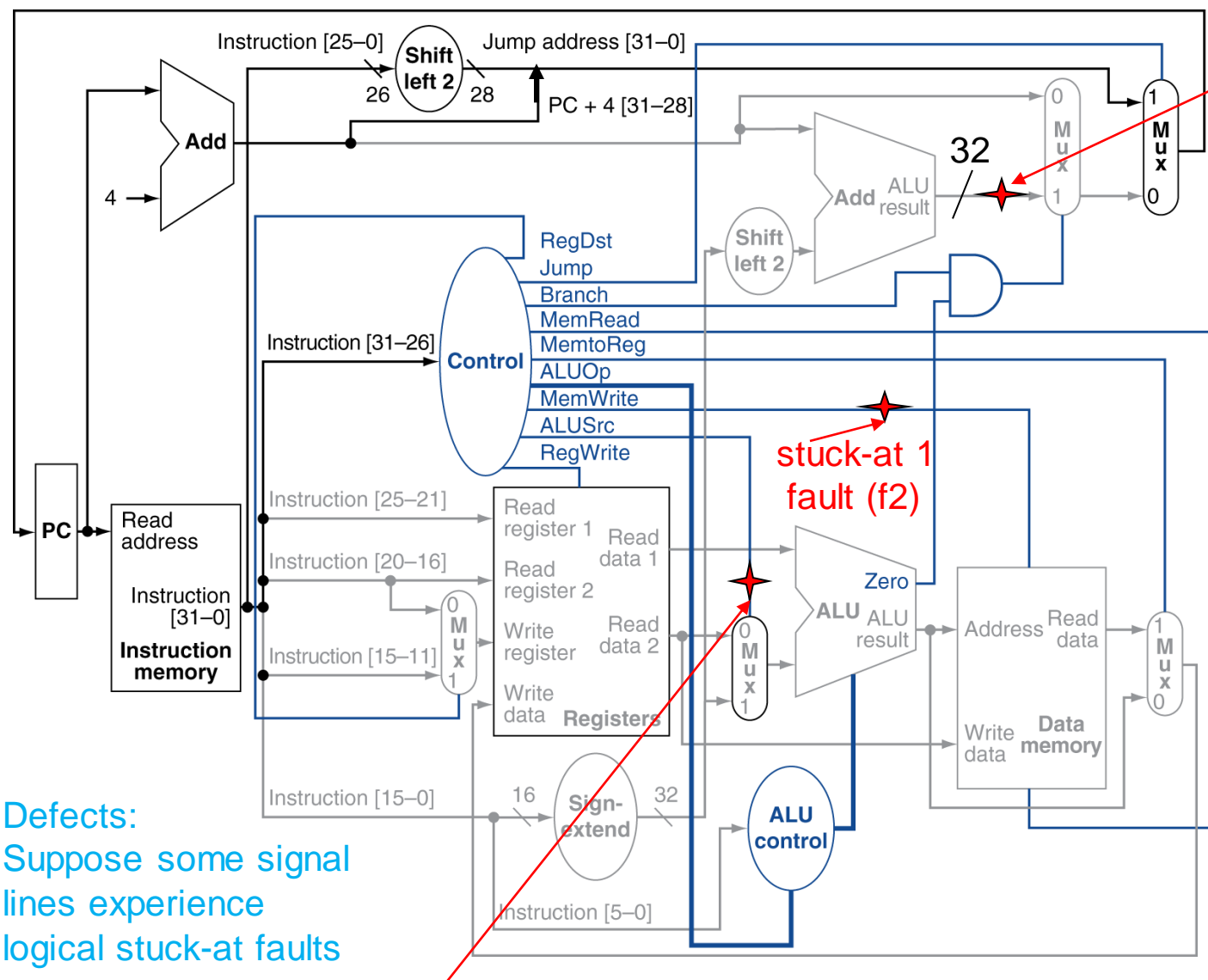In MIPS, programs typically start at memory address 0x00400000



Defects:
Suppose some signal
lines experience
logical stuck-at faults

stuck-at 0 fault (f1)

LSB is stuck-at 1 (f3)

In the presence of f1:
ADD, SUB, AND, OR,
SLT ✓


BEQ, JUMP ✓

ADDI, SUBI,
LW, SW ✗

In the presence of f2: ?

In the presence of f3: ?
Catastrophic! Why?

Timing Faults in MIPS Processor

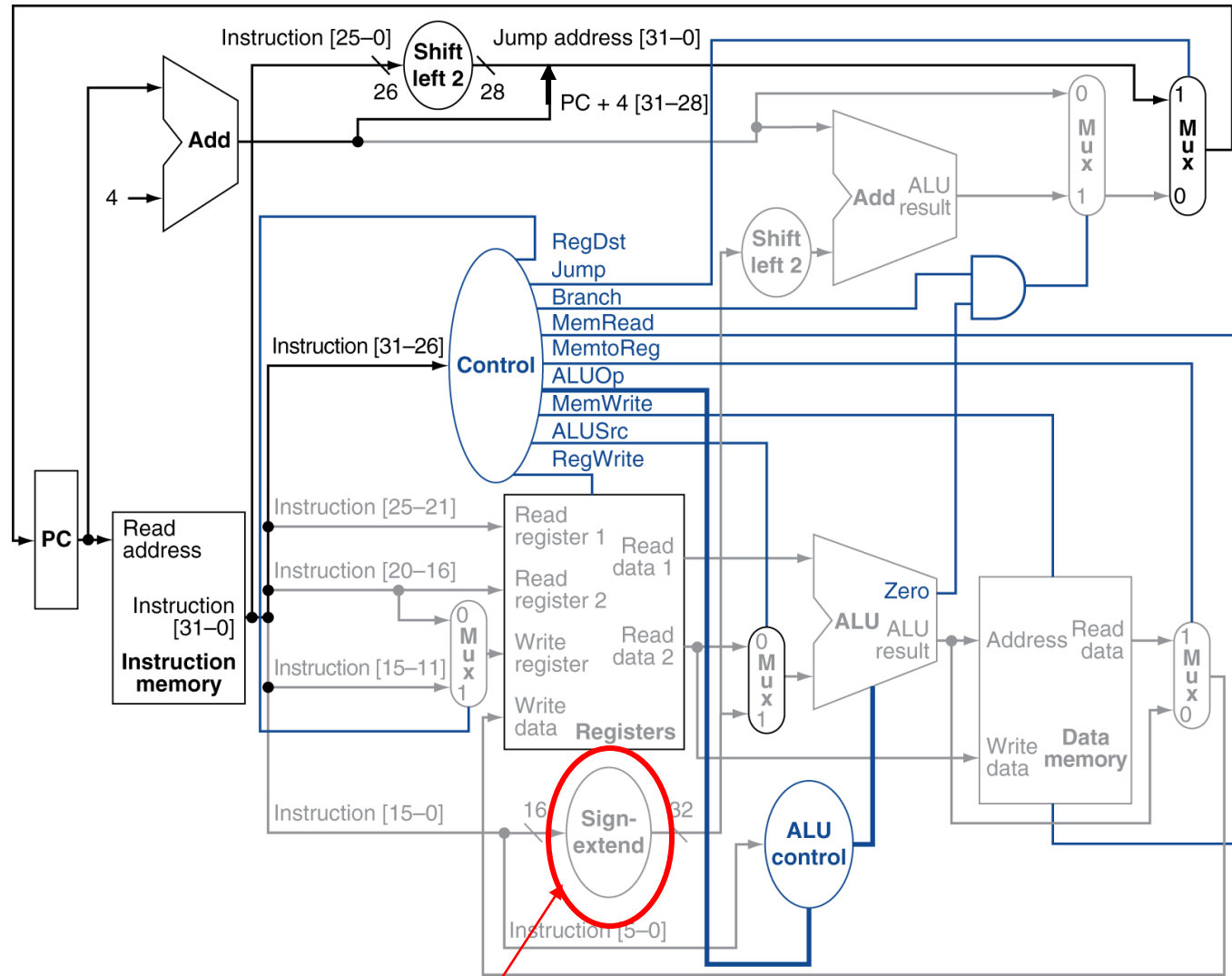

delay fault

Defects:
Suppose Sign-Ext.
Unit has become
slower than usual;
How to test if it is
impacting outputs?

May be we can try:

AND \$r1, \$r2, \$zero
ADDI \$r1, \$zero, 5
li \$v0, 1
MOVE \$a0, \$r1
Syscall

Check output to
ascertain
if the SE-block is slow
beyond tolerance